 


CDA Computer Logic Design


Homework 3

Points: 100



- 1) Implement the below logic circuit by using only NAND gates. (Do not simplify except to delete two inverters in series, if any) (15 points)



 
- 2) a) Find the hazards in the below circuit (5 points)
b) Modify the circuit so that it is hazard free (10 points)



  - 3) Complete the timing diagram for the given circuit. Assume that all gates have a propagation delay of 1 ns (10 points)



 - 4) Implement a full adder
- using two 8-to-1 MUXes. Connect X,Y, and Cin to the control inputs of the MUXes and connect 1 or 0 to each data input. (5 points)
 - using two 4-to-1 MUXes and one inverter. Connect X and Y to the control inputs of the MUXes, and connect 1's, 0's, Cin, or C'in to each data input. (5 points)
 - again using two 4-to-1 MUXes, but this time connect Cin and Y to the control inputs of the MUXes, and connect 1's, 0's, X, or X' to each data input. Note that in this fashion, any N-variable logic function may be implemented using a 2(N-1)-to-1 MUX. (5 points)
- 5) The circuit below has a 2-to-4 decoder with active high outputs connected to a 4-to-1 MUX with an active low output. Derive a minimum SOP or a minimum POS expression for the output, f(A, B, C, D). (15 points)



- 6) Show how to make an 8-to-1 MUX using a PAL. Assume that PAL has 14 inputs and six outputs and assume that each output OR gate may have up to four AND terms as inputs, as in Figure 9-33. (Hint: Wire some outputs of the PAL around to the inputs, external to the PAL. Some PALs allow this inside the PAL to save inputs.) (15 points)
- 7) The following PLA will be used to implement the following equations:
- $$X = AB'D + A'C' + BC + C'D'$$
- $$Y = A'C' + AC + C'D'$$
- $$Z = CD + A'C' + AB'D$$
- Indicate the connections that will be made to program the PLA to implement these equations. (7 points)
 - Specify the truth table for a ROM which realizes these same equations. (8 points)

