

NAME: SOLUTIONS

UNumber: _____

Computer Logic Design

Duration: 75 Minutes

CDA 3201

September 29, 2016

Closed Book, Notes, HW

Exam 1

R. Kasturi

One sheet of Letter size paper written on front and back is allowed.

SHOW ALL WORK TO GET PARTIAL CREDIT. MAKE REASONABLE ASSUMPTIONS.

I (One point each) Answer True or False. Unless otherwise noted, all numbers are in decimal.

- T a. If a Boolean expression is false its dual must also be false.
- T b. Quine-McCluskey method is guaranteed to find the most minimized Sum of Products expression.
- T c. For a function of three binary variables, $\sum m(1,3,6,7) + \sum d(0,2)$ and $\prod M(4,5) \cdot \prod D(0,2)$ have identical truth tables.
- F d. Every *Don't Care* term must be covered by at least one of the terms of the resulting Boolean expression.
- F f. A truth table implemented by its *Canonical Product of Sums* form must have the same number of literals as its *Canonical Sum of Products* implementation.
- F e. An N-Channel MOS transistor forms a conducting channel when its gate is negative with respect to its source.
- F g. The minimized Boolean expression for any function obtained from Quine McCluskey method must include every variable in its true or complement form.
- F h. $(011)_2 \times (011)_2 \times (011)_2 = (0111111)_2$ where \times denotes multiplication operation.
- T i. When representing positive values, $(4077)_8 = (83F)_{16}$
- T j. $\overline{[A(\overline{AB})]} \cdot \overline{[B(\overline{AB})]} = \overline{AB} + \overline{AB}$

NAME: SOLUTIONS

UNumber:

Computer Logic Design

Duration: 75 Minutes

Exam 1 CDA 3201

September 29, 2016

II (10 points) Use the Quine-McCluskey Method to find the minimum sum of products form for the Boolean expression $F(W, X, Y, Z) = \Sigma m(0, 4, 5, 8, 9, 13) + \Sigma d(2, 7, 15)$. Identify Essential Prime Implicants, if any.

QUINE-McCLUSKEY IMPLICATION TABLE

Minterm	Column 1	Column 2	Column 3
0	0000✓		
2	0010✓	00-0*	
4	0100✓	0-00*	
8	1000✓	-000*	
5	0101✓	010-*	
9	1001✓	100-*	
7	0111✓	01-1✓	-1-1*
13	1101✓	-101✓	
15	1111✓	1-01*	
		-111✓	
		11-1✓	

WX \ YZ	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

CROSSCHECK WITH
K-MAP
 $XZ + \overline{W}\overline{Y}\overline{Z} + W\overline{X}\overline{Y}$

Prime Implicant Chart

MINTERMS	0	4	5	8	9	13
5, 7, 13, 15 -1-1	-	-	*	-	-	*
0, 2 00-0	*					
0, 4 0-00	*	*	-	-	-	-
0, 8 -000	*			*		
4, 5 010-		*	*			
8, 9 100-	-	-	-	*	*	-
9, 13 1-01					*	*
COVERED ? →	✓	✓	✓	✓	✓	✓

✓
THERE
ARE
NO
EPIs

Final Boolean Expression, $F(WXYZ) = XZ + \overline{W}\overline{Y}\overline{Z} + W\overline{X}\overline{Y}$

THIS PROVIDES MINIMAL COVER

NAME: SOLUTIONS

UNumber: _____

Computer Logic Design


Duration: 75 Minutes

Exam 1 CDA 3201

September 29, 2016


III (a) (5 points) Using K-map find the simplified Boolean expression for the function
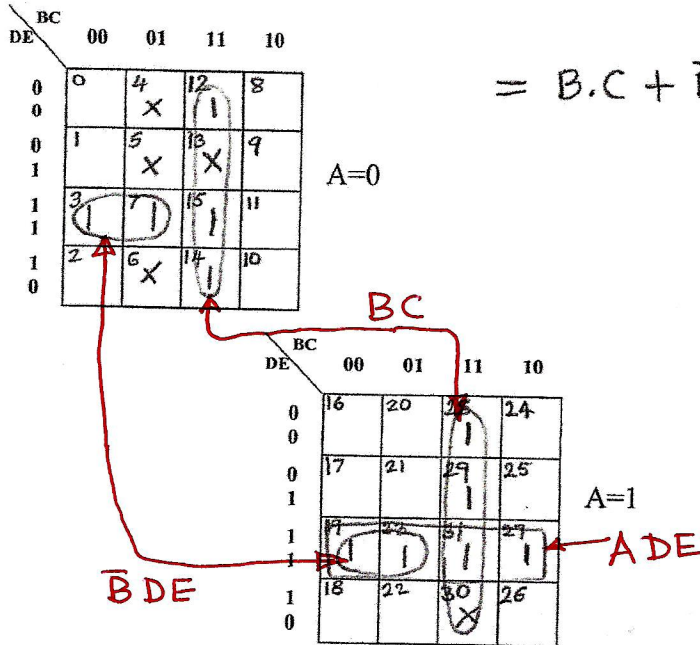
$$F(A, B, C, D, E) = \sum m(3, 7, 12, 14, 15, 19, 23, 27, 28, 29, 31) + \sum d(4, 5, 6, 13, 30)$$




$$= B.C + \bar{B}.D.E + A.D.E$$

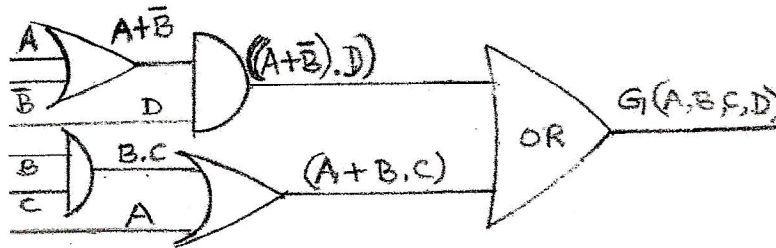(b) (i) (2 points) Draw the gate level diagram for the multi-level function exactly as expressed here (i.e., do not expand or simplify): $G(A, B, C, D) = ((A + \bar{B}) . D) + (A + B . C)$



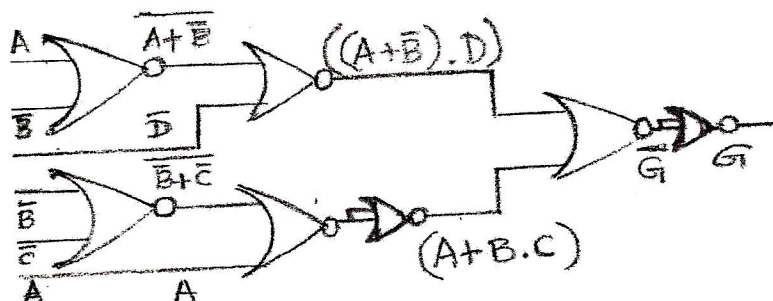(ii) (3 points) Redraw the function (do not expand or simplify) using only NORs:



NAME: SOLUTIONS

UNumber: _____

Computer Logic Design

Duration: 75 Minutes

Exam 1 CDA 3201


September 29, 2016

- IV (a) (6 points) Days of the week are represented using three bits as shown in the table. An alarm circuit is enabled and rings a bell each day of the week at 7 AM but you want to disable it on the weekend. Complete the Truth Table representing disabled alarm on Saturday and Sunday by 0; derive the minimized **product of sums (POS)** binary expression for the alarm. Draw the corresponding gate level diagram. Assume that the variables are available in both True and Complement form.

B ₂	B ₁	B ₀	DAY	ALARM
0	0	0	SUN	0
0	0	1	MON	1
0	1	0	TUE	1
0	1	1	WED	1
1	0	0	THU	1
1	0	1	FRI	1
1	1	0	SAT	0
1	1	1	--	X

	B ₂ B ₁			
	00	01	11	10
B ₀	0	1	0	1
	1	1	X	1
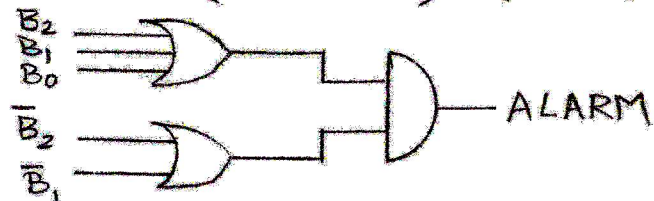
$$\text{ALARM} = (B_2 + B_1 + B_0) \cdot (\bar{B}_2 + \bar{B}_1)$$



- (b) (4 points) Show the arrangement of CMOS transistors to realize the function $\overline{((A \cdot B + C) \cdot D)}$

