

NAME: \_\_\_\_\_ SOLUTIONS \_\_\_\_\_ UNumber: \_\_\_\_\_ Computer Logic Design  
Duration: 75 Minutes CDA 3201 October 1, 2015  
Closed Book, Notes, HW Exam 1 R. Kasturi  
One sheet of Letter size paper written on front and back is allowed.  
SHOW ALL WORK TO GET PARTIAL CREDIT. MAKE REASONABLE ASSUMPTIONS.

I (One point each) Answer True or False. Unless otherwise noted, all numbers are in decimal.

- \_T\_ a. An *Essential Prime Implicant* must include at least one element of the on-set that is not covered by any other implicant.
- \_T\_ b. For any given Boolean Expression, there is one and only one Truth Table.
- \_T\_ c. The Boolean expression  $\overline{A \cdot B} + \overline{\overline{A} \cdot \overline{B}}$  represents the output of a two-input Exclusive OR gate.
- \_F\_ d. The sum of a negative number in 8 bit sign-magnitude form and the same number in its 8 bit two's complement form results in all 8 bits becoming 0.
- \_F\_ f. A NOR gate cannot be implemented using only NAND gates.
- \_T\_ e. In a 6-bit Twos-Complement representation,  $-27 = (100101)_2$ .
- \_T\_ g.  $(A + B + C + D) = \overline{(\overline{A + C})(\overline{B + D})}$ .
- \_T\_ h. The sign-magnitude representation of a positive number N and the corresponding negative number (-N) differ only in one bit.
- \_T\_ i. A P-Channel MOS transistor forms a conducting channel when its gate is negative with respect to its source.
- \_F\_ j. Carry-lookahead circuit increases the carry propagation time of the corresponding ripple carry adder.

II (10 points) Use the Quine-McCluskey Method to find the minimum sum of products form for the Boolean expression  $F(A, B, C, D) = \Sigma m(0, 2, 8, 10, 11, 13, 14, 15) + \Sigma d(3, 4)$

QUINE-McCLUSKEY IMPLICATION TABLE

Minterms	Column 1	Column 2	Column 3
0	0000✓	00_0✓	
		0_00*	-0_0*
2	0010✓	-000✓	
4	0100✓	001_✓	
8	1000✓	-010✓	
		10_0✓	-01_*
3	0011✓	-011✓	
10	1010✓	101_✓	1_1_*
11	1011✓	1_10✓	
13	1101✓	1_11✓	
14	1110✓	11_1*	
15	1111✓	111_✓	

PRIME IMPLICANT CHART

Minterms	0	2	8	10	11	13	14	15	
Prime Implicants									
0, 2, 8, 10	* -	* -	⊗ -	* -	-	-	-	-	EPI
2, 3, 10, 11		*		*	*				NOT NEEDED
10, 11, 14, 15				* -	* -	-	⊗ -	* -	EPI
0, 4	*								NOT NEEDED
13, 15						⊗ -	-	* -	EPI

FINAL BOOLEAN EXPRESSION:  $F = \overline{B}\overline{D} + AC + ABD$

NAME: \_\_\_\_\_

UNumber: \_\_\_\_\_

Computer Logic Design



Duration: 75 Minutes

Exam 1 CDA 3201

October 1, 2015

III Consider a function  $F(A, B, C, D, E)$  as described by the K-Map below. The input variables are available in both True and Complement form.

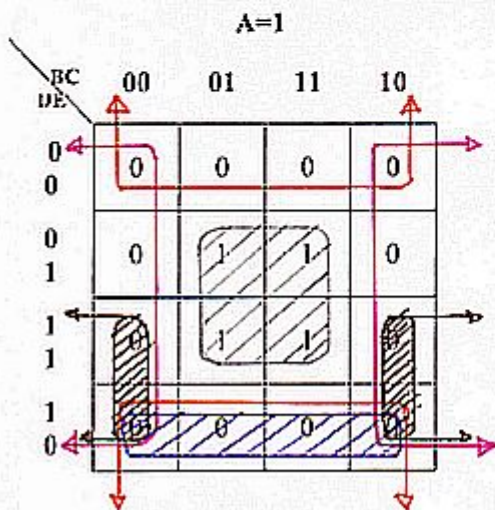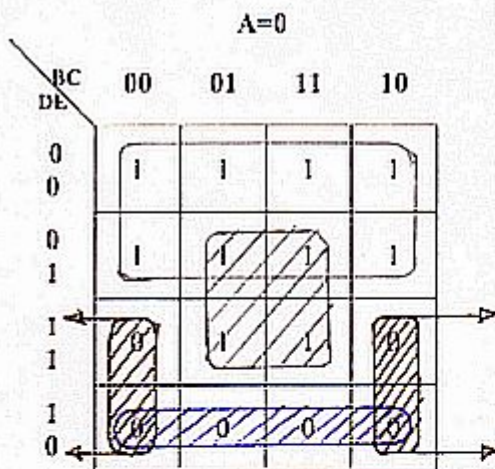
- (3 points) Find the minimized Product of Sums expression of  $F$ .
- (2 points) Implement the PoS using only NOR gates.
- (3 points) Find the minimized Sum of Products expression of  $F$ .
- (2 points) Implement the SoP using only NAND gates.



Note that Shaded regions Connect Implicants on the top ( $A=0$ ) and bottom ( $A=1$ ) figures.


$$a. F = (C + \bar{D})(\bar{D} + E)(\bar{A} + E)(\bar{A} + C)$$
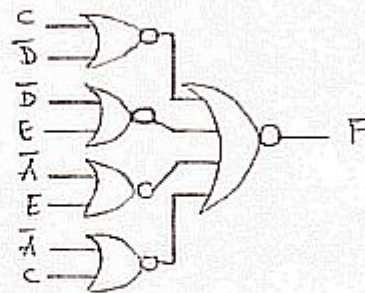
$$b. F = \frac{(C + \bar{D})(\bar{D} + E)(\bar{A} + E)(\bar{A} + C)}{(C + \bar{D}) + (\bar{D} + E) + (\bar{A} + E) + (\bar{A} + C)}$$




$$c. F = \bar{A}\bar{D} + CE$$
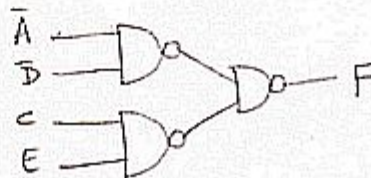
$$d. F = \frac{\bar{A}\bar{D} + CE}{\bar{A}\bar{D} \cdot CE}$$



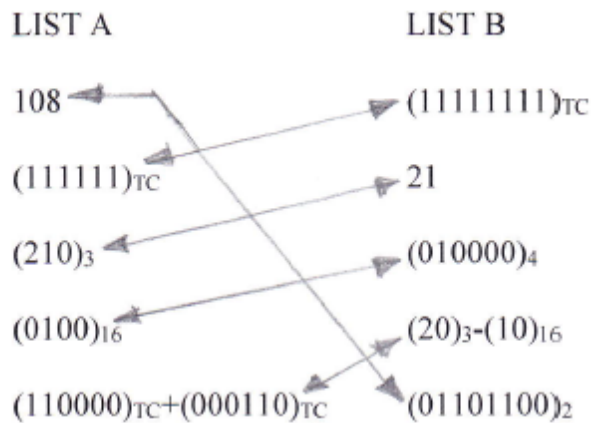IV (a) Draw lines connecting items on list A to their corresponding items with same value in list B. Subscript TC indicates *Twos-Complement* representation. Numbers without subscripts are in Decimal notation.



(b) (5 points) Show the arrangement of CMOS transistors to realize the function  $\overline{(A \cdot B) + C + D}$

