

FIVE STAR

Homework #1

Steven Romeiro

Question 1:

a) 100010

$$\begin{array}{r} 111\ 000 \\ 001\ 101 \\ \hline (110011)_2 \end{array}$$

True

$$(110011)_2 = (110011)_2$$

b) $\begin{array}{r} 28 \\ 705 \\ -5274 \\ \hline (2011)_8 \end{array}$

True

$$(2011)_8 = (2011)_8$$

c) $\begin{array}{r} 100 \\ 1100 \longdiv{110011} \\ -1100 \\ \hline 000011 \end{array}$

False

$$(11)_2 \neq (10)_2$$

d) $5E2$

$$\begin{array}{r} F04 \\ \times 1788 \\ \hline 000 \end{array}$$

True

$$(585588)_{16} = (585588)_{16}$$

583E
585588

e) Conversion $(1011.101)_2 = (11.5)_8$

$$\begin{array}{r} \underbrace{001}_{1} \underbrace{011}_{3.} \underbrace{101}_{5} \\ \rightarrow \boxed{(13.5)_8 \neq (11.5)_8} \end{array} \quad \text{False}$$

f) Conversion $(1011.1101)_2 = (C.B)_{16}$

$$\begin{array}{r} \underbrace{1011}_{B} \underbrace{.1101}_{D} \\ \rightarrow \boxed{(B.D)_{16} \neq (C.B)_{16}} \end{array} \quad \text{False}$$

g) Conversion $(5752.777)_8 = (BEA.FFF)_{16}$

$$\begin{array}{r} \overbrace{101}^5 \overbrace{111}^7 \overbrace{101}^5 \overbrace{010}^2 \cdot \overbrace{111}^7 \overbrace{111}^7 \overbrace{111}^7 \\ \text{B E A F F 8} \end{array}$$

$$\begin{array}{r} \underbrace{1011}_{B} \underbrace{1110}_{E} \underbrace{1010}_{A} \cdot \underbrace{1111}_{F} \underbrace{1111}_{F} \underbrace{1000}_{8} \\ \text{B E A F F 8} \end{array}$$

$$\begin{array}{r} \boxed{(BEA.FFF)8 \neq (BEA.FFF)16} \\ \text{False} \end{array}$$

h) DeMorgan's Law is limited to 2 variables:

False

FIVE STAR®

FIVE STAR®

FIVE STAR®

FIVE STAR®

Question 2:

a) Hex $(1FB)_{16}$ to decimal:

1 F B

$$\begin{array}{r} 0001\ 1111\ 1011 \\ \hline \end{array} \rightarrow 1 + 2 + 8 + 16 + 32 + 64 + 128 + 256 = \boxed{(267)_{10}}$$

b) Octal $(374)_8$ to binary:

3 7 4

011 111 100

$$\rightarrow \boxed{(11111100)_2}$$

c) Binary $(10111110110)_2$ to Hex:

1011 1111 0110

B

F

6

$$\rightarrow \boxed{(BF6)_{16}}$$

d) Decimal $(627)_{10}$ to trinary:

$$\begin{array}{r} 3\sqrt{627} = 209 R0 \rightarrow 3\sqrt{209} = 69 R2 \rightarrow 3\sqrt{69} = 23 R0 \\ -\frac{6}{027} \\ \hline -\frac{18}{29} \\ \hline 27 \end{array}$$

$$3\sqrt{23} = 7 R2 \rightarrow 3\sqrt{7} = 2 R1 \rightarrow 3\sqrt{2} = 0 R2$$

$$-\frac{21}{2}$$

$$\boxed{(212020)_3}$$

e) What is the base x in $(2400)_x = (1010)_7$

$$\begin{array}{cccc} 7^3 & 7^2 & 7^1 & 7^0 \\ \hline 343 & 49 & 7 & 1 \end{array}$$

$$\begin{array}{cccc} 5^3 & 5^2 & 5^1 & 5^0 \\ \hline 125 & 25 & 5 & 0 \end{array}$$

$$1 \cdot 343 + 0 \cdot 49 + 1 \cdot 7 + 0 \cdot 1 = (350)_{10} \quad 2 \cdot 125 + 4 \cdot 25 + 0 \cdot 5 + 0 \cdot 5 = (350)_5$$

X is radix or base 5

Question 3:

a) 8 bits required

$$\begin{array}{r} 01001011 \quad (+75)_{10} \\ +11100000 \quad (-32)_{10} \\ \hline (00101011)_2 \quad (+43)_{10} \\ \boxed{(00101011)_2} \end{array}$$

$$\begin{array}{r} 11000111 \quad (-57)_{10} \\ +0111001 \quad (+99)_{10} \\ \hline (00101010)_2 \quad (+42)_{10} \\ \boxed{(00101010)_2} \end{array}$$

$$\begin{array}{r} 11001100 \quad (-52)_{10} \\ +01010100 \quad (-84)_{10} \\ \hline 01111000 \quad (+120)_{10} ? \end{array}$$

$(01111000)_2$ is incorrect
due to overflow. We
exceeded our available bits

FIVE STAR

FIVE STAR

FIVE STAR

FIVE STAR

$$b4) \quad 37 + 93 \rightarrow \begin{array}{r} 0\ 0\ 1\ 0\ 0\ 1\ 0\ 1 \\ + 0\ 1\ 0\ 1\ 1\ 1\ 0\ 1 \\ \hline 1\ 0\ 0\ 0\ 0\ 0\ 1\ 0 \end{array} \quad (+37)_0 \quad (+93)_0 \quad (-126)_0 ?$$

(10000010)₂ is the incorrect answer due to overflow. The sign bit was changed when addition of two positive numbers exceeded the available bits

Question 4:

a) Simplify $XY + XY'$
 $X(Y + Y')$

b) $(X+Y)(X+Y') = X + (Y \cdot Y') = \boxed{X}$ Rule
 $A + (BC) = (A+B)(A+C)$

c) $Y'Z + X'YZ + XYZ$
 $(YZ)(X+X') + Y'Z$
 $(YZ) + Y'Z$
 $Z(Y + Y')$

$$d) (x+y)(x'+y+z)(x'+y+z)$$

Rule $x \cdot x = x$

$$(x+y)(x'+y+z)$$

Distributive

$$xx' + XY + YX' + XZ + YY + YZ$$

Rule $XY + YX' = Y$

$$XY' + Y + YZ + XZ$$

Rule $Y + YZ = Y$

$$XY + Y + XZ$$

Rule $Y + XY = Y$

$$\boxed{Y + XZ}$$

$$e) x + XYZ + X'YZ + X'Y + \underline{wx + wx'}; \text{ Rule } XY + X'Y = X$$

$$x + \underline{XYZ} + \underline{X'YZ} + X'Y + w; \text{ Rule } XY + X'Y = X$$

$$x + \underline{YZ} + \underline{X'Y} + w;$$

Rule $(XY) + (Z Y) = Y(X+Z)$

$$x + Y(Z + X')$$

distribute

$$\underline{x} + \underline{X'Y} + YZ + w$$

Rule $X + (X'Y) = X + Y$ Elim

$$x + Y + YZ + w$$

Rule $Y + YZ = Y$ Absorption

$$\boxed{X + Y + w}$$

FIVE STAR

FIVE STAR

FIVE STAR

FIVE STAR

Question 5:

$$A = 10110110$$

$$B = 11001000$$


a) $\text{NAND} = [(A)(B)]' = [(10110110)(11001000)]'$
 $= (10000000)' = \boxed{01111111}$


b) $\text{NOR} = [(A)+(B)]' = [(10110110)+(11001000)]'$
 $= (01001001)(00110111) = \boxed{00000001}$

c) $\text{XOR} = (10110110) \oplus (11001000)$
 $= \boxed{0111110}$

Question 6:

a)

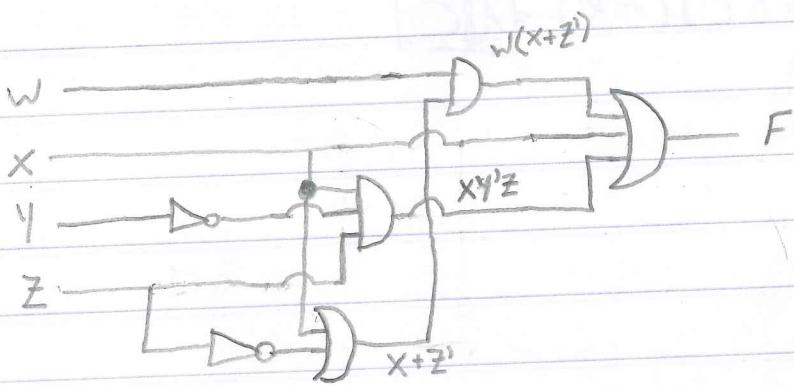

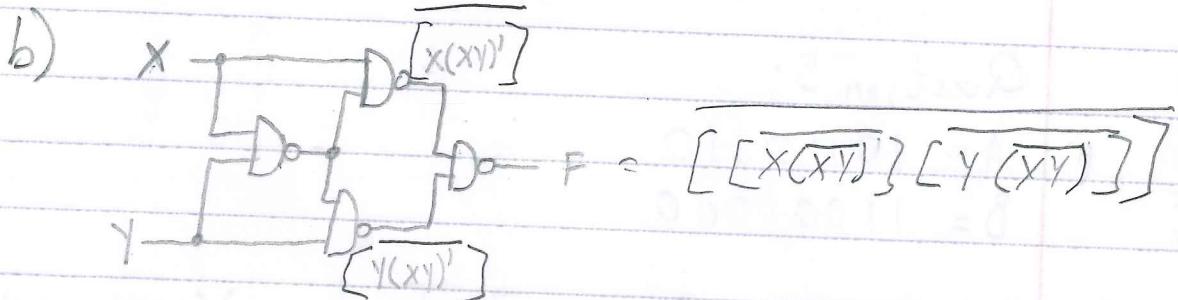

$$\begin{aligned}
 F &= \overline{[\overline{X(XY)}][\overline{Y(XY)}]} = \overline{\overline{X(XY)}} + \overline{\overline{Y(XY)}} \\
 &= \overline{X(XY)} + \overline{Y(XY)} = \overline{X(X'+Y')} + \overline{Y(X'+Y')} \\
 &= \overline{XX'} + \overline{XY'} + \overline{YX'} + \overline{YY'} = \boxed{\overline{XY} + \overline{X'Y}}
 \end{aligned}$$

Question 7:

a) $((A'+B)(C'+D))' = (A'+B)' + (C'+D)'$
 $= (A'+B) + (C'+D) = \boxed{A'+B+C'+D'}$

b) $((AB'C) + (AB'))' = (AB'C)'(AB')'$
 $= (AB'C)(AB') = \boxed{ABC}$


Question 8:

$K = \text{Kyle}$, $P = \text{Patrick}$, $J = \text{Jorge}$, $S = \text{Steven}$

$M = \text{Marshall Center}$, $D = \text{Juniper}$


K	P	J	S	OUTPUT
0	0	0	0	0 $\rightarrow J \& S \text{ Agree}$
0	0	0	1	0 $\rightarrow \text{Majority}$
0	0	1	0	0 $\rightarrow \text{Majority}$
0	0	1	1	1 $\rightarrow J \& S \text{ Agree}$
0	1	0	0	0 $\rightarrow J \& S \text{ Agree}$
0	1	0	1	0 $\rightarrow \text{Tie}$
0	1	1	0	0 $\rightarrow \text{Tie}$
0	1	1	1	1 $\rightarrow J \& S \text{ Agree}$
1	0	0	0	0 $\rightarrow J \& S \text{ Agree}$
1	0	0	1	0 $\rightarrow \text{Tie}$
1	0	1	0	0 $\rightarrow \text{Tie}$
1	0	1	1	1 $\rightarrow J \& S \text{ Agree}$
1	1	0	0	0 $\rightarrow J \& S \text{ Agree}$
1	1	0	1	1 $\rightarrow \text{Majority}$
1	1	1	0	1 $\rightarrow \text{Majority}$
1	1	1	1	1 $\rightarrow J \& S \text{ Agree}$
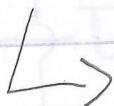
$$K'P'JS + K'PJS + KP'JS + KPJS + KPJ'S + KPJS'$$




$$\begin{aligned}
 & K'P'JS + K'PJS + KP'JS + KPJ'S + KPJS' + KPJS \\
 & PJS(K+K') + K'P'JS + KP'JS + KPJ'S + KPJS \\
 & PJS + K'P'JS + KP'JS + KPJ'S + KPJS \\
 & JS(P+K'P'+KP') + KP(J'S+JS') \\
 & JS(P+P') + KP(J'S+JS') \\
 & \boxed{JS + KP(J \oplus S)}
 \end{aligned}$$

		JS	00	01	11	10
		KP	00	01	11	10
00	00		0	0	1	0
			0	0	1	0
11	01	0	1	1	1	1
		0	1	1	1	1
10	10	0	0	1	0	0
		0	0	1	0	0

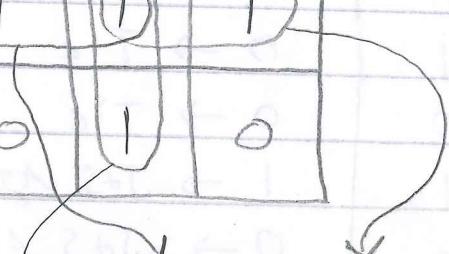


$$\boxed{JS + KPS + KPJ}$$

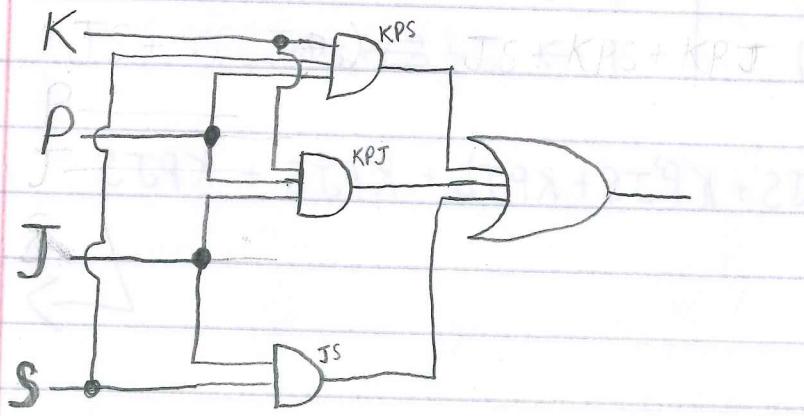


Steven Romano

Homework 2

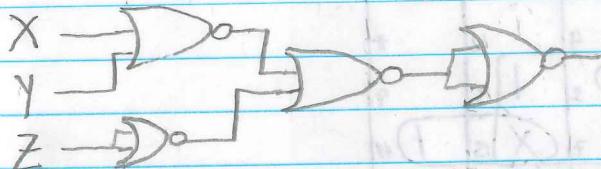① a) $\overline{(x+y)} + z' \equiv \overline{(x+y)} + \overline{z}$



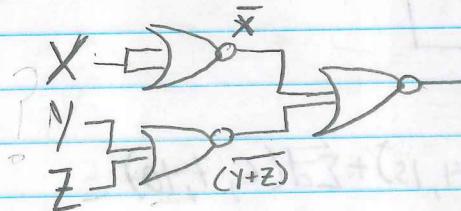
b) $xy + xz \equiv x(y+z) \equiv x + \overline{(y+z)}$



② a) $\overline{(x+y)} + z' \equiv \overline{(x'y')} + \overline{z} \equiv \overline{(x'y')} \cdot \overline{z}$



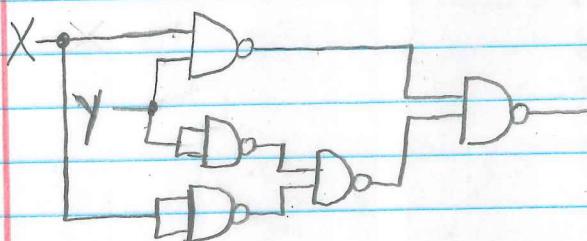b) $xy + x'y' \equiv \overline{(xy + x'y')} \equiv \overline{(xy)} \cdot \overline{(x'y')}$



circled marks

So there are 10

③ a) $f(a, b, c, d) = \sum_m(1, 7, 11, 13) + \sum_d(2, 5, 14, 15)$

cd \ ab	00	01	11	10
00	0	X 4	1 12	8
01	1	(X) 5	1 13	9
11	3	1 7	(X) 15	11
10	X 2	6	X 14	10

$$= [bd + a'c'd + acd]$$

b) $f(a, b, c, d) = \prod_m(1, 2, 11, 13, 14, 15) + \sum_d(6, 7, 10)$

cd \ ab	00	01	11	10
00	1 0	1 4	1 12	(1) 8
01	0 1	1 5	0 13	(1) 9
11	1 3	(X) 7	0 15	0 11
10	0 2	(X) 6	0 14	X 10

$$a'b + c'd' + a'cd + ab'c'$$

	xx	00	01	11	10
yy	00	01	11	10	
	00	01	11	10	
$F_3 =$	00	01	11	10	
	00	01	11	10	

	xx	00	01	11	10
yy	00	01	11	10	
	00	01	11	10	
$F_2 =$	01	00	11	10	
	01	00	11	10	

	xx	00	01	11	10
yy	00	01	11	10	
	00	01	11	10	
$F_1 =$	00	01	11	10	
	01	11	10	11	

(5)

Inputs

Possible Multiplications

$X_2 X_1 \cdot Y_2 Y_1$	0 · 0	1 · 0	2 · 0	3 · 0
0 · 0 · 0 0	0 · 1	1 · 1	2 · 1	3 · 1
0 1 · 0 1	0 · 2	1 · 2	2 · 2	3 · 2
1 0 · 1 0	0 · 3	1 · 3	2 · 3	3 · 3
1 1 · 1 1				

Need 4-bit output - $F = \text{OUTPUT}$

$$F_4 = X_1 X_2 Y_1 Y_2$$

X	Y	F_{4-1}	X	Y	F_{4-1}
00 · 00	0000	10 · 00	0000		
00 · 01	0000	10 · 01	0010		
00 · 10	0000	10 · 10	0100		
00 · 11	0000	10 · 11	0110		
01 · 00	0000	11 · 00	0000		
01 · 01	0001	11 · 01	0011		
01 · 10	0010	11 · 10	0110		
01 · 11	0011	11 · 11	1001		

$$F_5 = X_2 Y_2 \bar{Y}_1 + X_2 \bar{X}_1 Y_2$$

$$F_2 = \bar{X}_2 X_1 Y_2 + X_1 Y_2 \bar{Y}_1 + X_2 \bar{Y}_2 Y_1 + X_2 \bar{X}_1 Y_1$$

$$F_1 = X_1 Y_1$$

(6) 5 inputs, output 1 when prime # of 1's in input

01011

 $F(A, B, C, D, E)$

10011

2 1's = 3, 5, 6, 9, 10, 12, 17, 18, 20, 24

00111

3 1's = 7, 11, 13, 14, 19, 21, 22, 25, 26, 28

01110

5 1's = 31

11100

11001

11010

10101

10110


10

$$\begin{aligned} F(A, B, C, D, E) &= A'B'DE + A'CD'E \\ &+ A'CDE' + A'BCD' + A'BDE' + A'BCE \\ &+ AB'C'E + AB'DE' + AB'CD' + AC'D'E \\ &+ ABC'D' + ABC'E' + ABCDE \end{aligned}$$


	DE	00	01	11	10
A=0	00	0	4	11	12
	01	1	5	11	13
	11	1	3	7	15
	10	2	6	11	10

	DE	00	01	11	10
A=1	00	16	17	20	21
	01	17	11	21	29
	11	1	19	23	31
	10	1	18	22	30
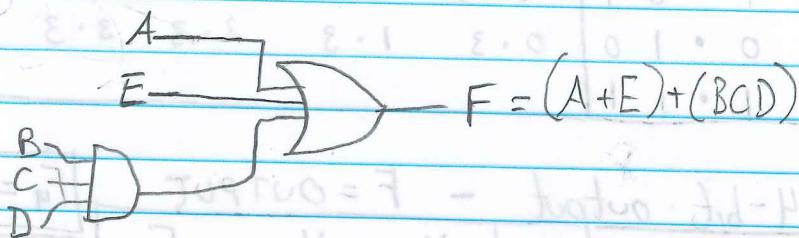
$$④ \text{ a) } [(A \cdot 1) + (A \cdot 1)] + E + [(BC) \cdot 1] \\ \equiv ((A \cdot 1) + E) + BCD \equiv (A + E) + BCD$$


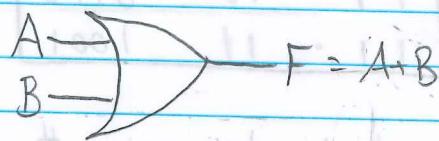
$$\text{b) } [(A \cdot B') + (AB + B)] B + A \\ \equiv [(A \cdot B') + B] B + A \equiv [(A + B) + B] B + A \\ \equiv (A + B)B + A \equiv B + A$$



$$\textcircled{7} \quad F(A, B, C, D) = \sum_m(0, 2, 5, 6, 7, 8, 10, 12, 13, 14, 15)$$

		AB		CD			
		00	01	11	10	01	11
00		0	4	7	12	1	5
01		1	5	11	13	9	
11		3	11	7	15	11	
10		7	2	11	19	11	

$$F(A, B, C, D) = BD + B'D' + BC + AB$$

$$\sum_m: 0000, 0010, 0101, 0110, 0111, 1000, 1010, 1100 \\ 1101, 1110, 1111$$

Groups 1 1's = 2, 8

2 1's = 5, 6, 10, 12

3 1's = 7, 13, 14

4 1's = 15

Groups	#	Column 1	#'	Column 2	#'	Column 3	*
0	0	0000✓	0, 2:	00-0✓	0, 2, 8, 10: -0-0		*
1	2	0010✓	0, 8:	-000✓			*
	8	1000✓					
	5	0101✓	2, 6:	0-10✓	2, 6, 10, 14: ---10		*
2	6	0110✓	2, 10:	-010✓	8, 10, 12, 14: 1---0		*
	10	1010✓	8, 10:	10-0✓			
	12	1100✓	8, 12:	1-00✓			
	7	0111✓	6, 14:	-110✓	6, 14, 7, 15: -11-		*
3	13	1101✓	10, 14:	1-10✓	12, 13, 14, 15: 11--		*
	14	1110✓	12, 13:	110-✓	5, 7, 13, 15: -1-1		*
4	15	1111✓	12, 14:	11-0✓			
			5, 7:	01-1✓			
			6, 7:	011-✓			
			7, 15:	-111✓			
			13, 15:	11-1✓			
			14, 15:	111-✓			





Prime Implicants Chart

\rightarrow (m) minterms	0	2	5	6	7	8	10	12	13	14	15
Prime Implicants	1	1	1	1	1	1	1	1	1	1	1
(0, 1, 2, 8, 10)	-	0	-	0	\textcircled{X}	X	1	1	X	X	1
(2, 6, 10, 14)	-	-	1	0	X	1	X	1	X	1	X
(8, 10, 12, 14)	1	-	-	0	1	1	1	X	X	X	1
(5, 7, 13, 15)	-	1	-	1	\textcircled{X}	1	X	1	X	1	X
(6, 14, 7, 15)	-	1	1	-	XX	X	1	1	X	X	1
(13, 14, 15)	1	1	-	-	X	X	X	X	X	X	1

$$F(A, B, C, D) = B'D' + BD + BC + AB$$



Homework 3

Esthaem Romeo

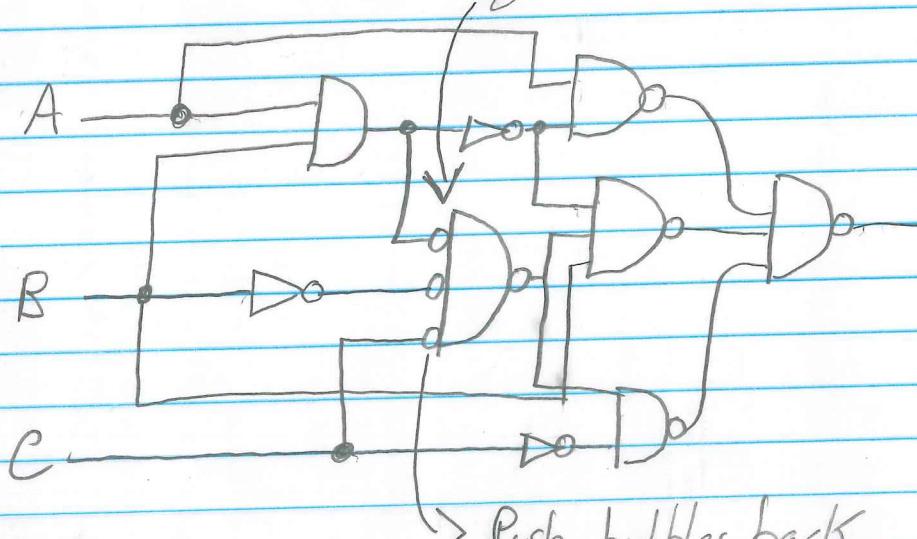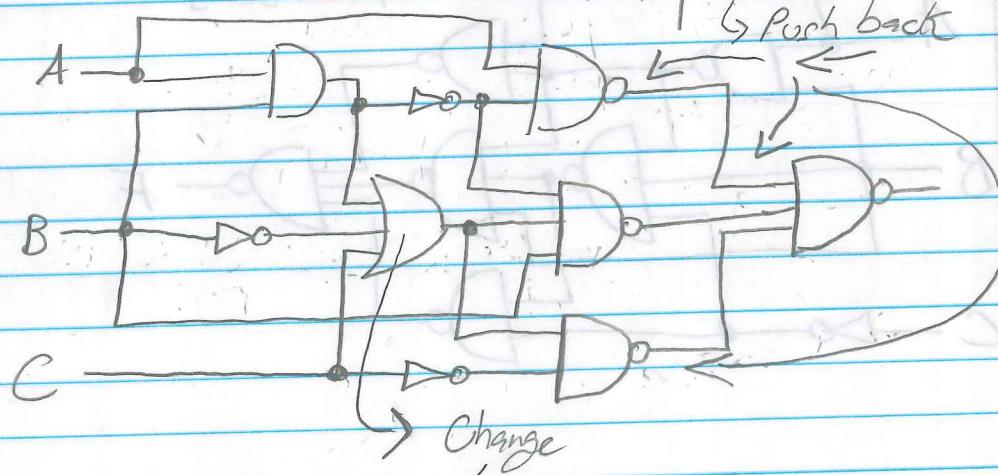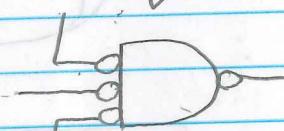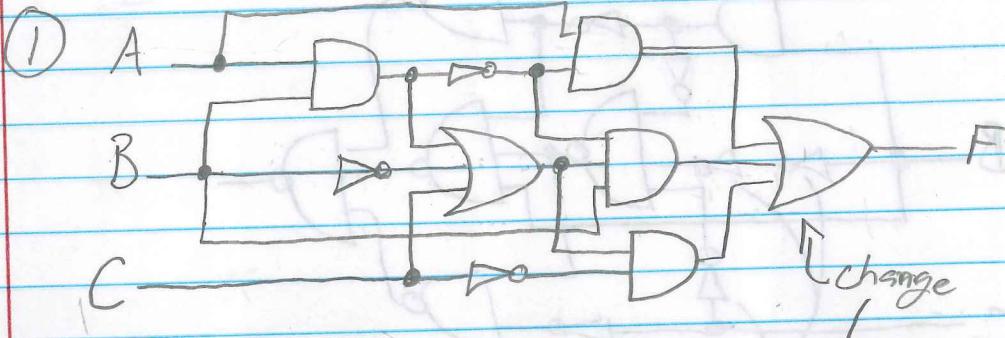


method part 2

Ethan Roth

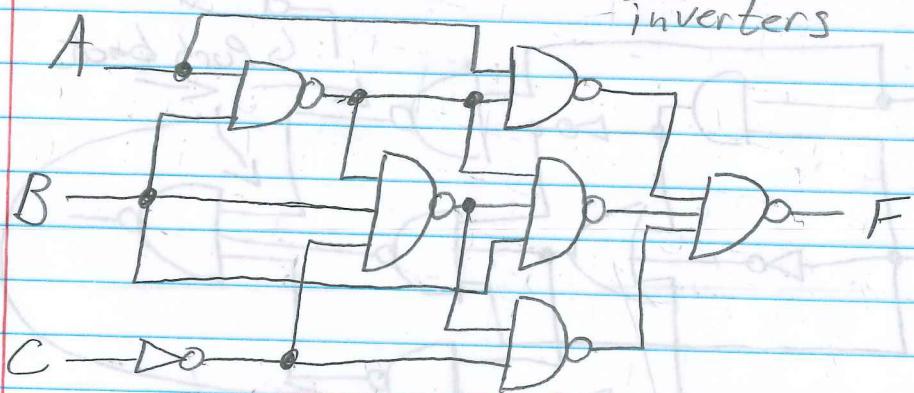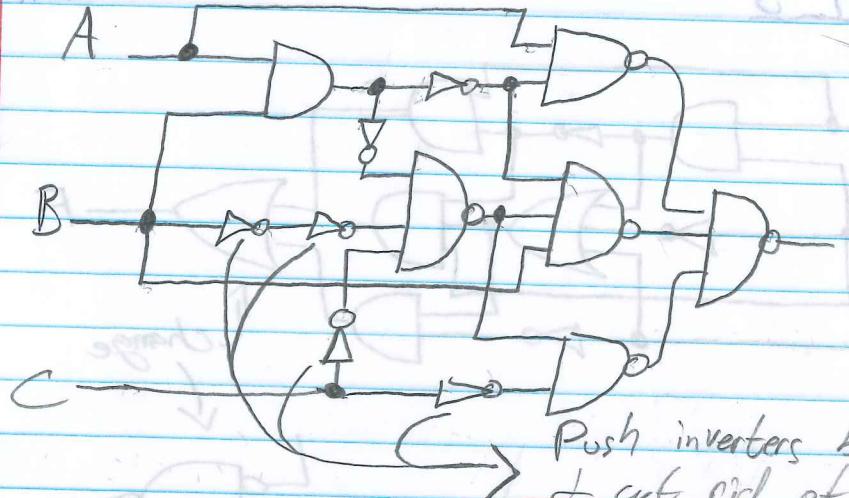

short without delay

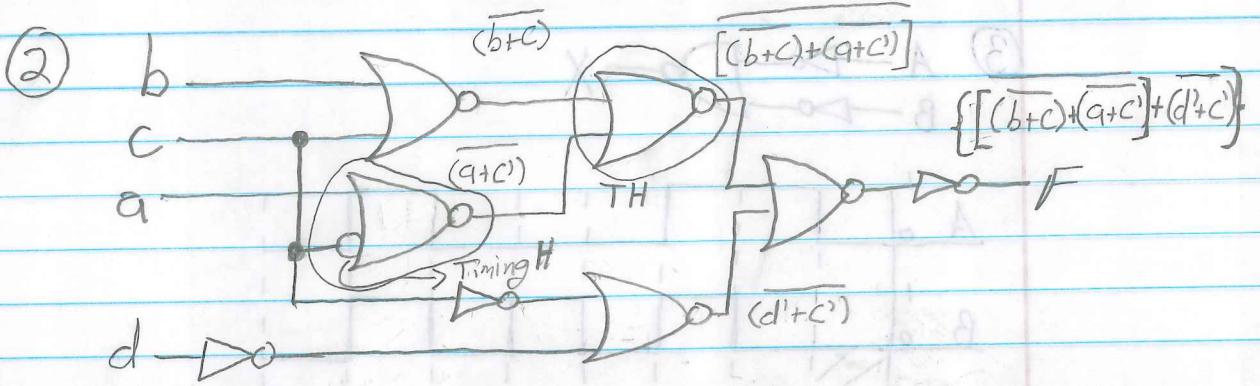

$$F = \{ \overline{[(b+c)+(a+c')]} + \overline{(d'+c')} \} = \{ \overline{[(b+c)(a+c')]} + \overline{(d'+c')} \}$$

$$= [(b+c)(a+c')] + (d'c) = [ba + bc' + ca + cc'] + dc$$

$$= [ba + bc' + ca] + dc = ba + bc' + ca + dc$$

$$ba = ba(c+c')(d+d') = abcd + abc'd + abcd' + abc'd'$$

$$bc' = bc'(a+a')(d+d') = abc'd + abc'd' + a'b'cd + a'b'cd'$$


$$ca = ca(b+b')(d+d') = abcd + abcd' + a'b'cd + a'b'cd'$$

$$dc = dc(a+a')(b+b') = abcd + a'b'cd + a'b'cd + a'b'cd$$

$$= abcd + abc'd + abcd' + abc'd' + a'b'cd + a'b'cd' + ab'cd \\ + ab'cd' + a'b'cd + a'b'cd$$




$\Sigma m(15, 13, 14, 12, 5, 4, 11, 10, 3, 7)$


cd	ab	00	01	11	10	
00						$\rightarrow bc' + ac + cd$
01						
11		1	1	1	1	
10		1	1	1	1	$\rightarrow ab$ to fix hazards

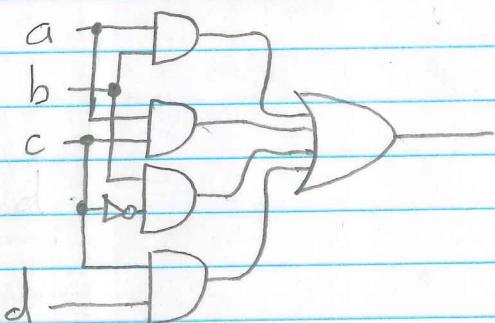



$$\textcircled{3} \quad A \rightarrow D_o \quad D_o - X$$

$$B \rightarrow D_o$$

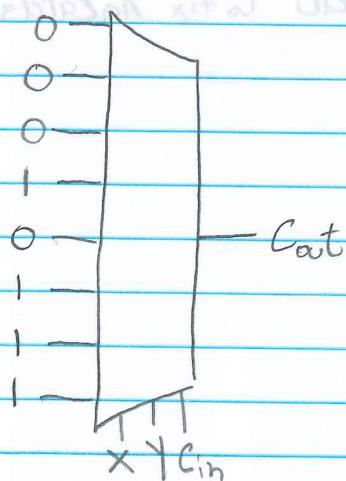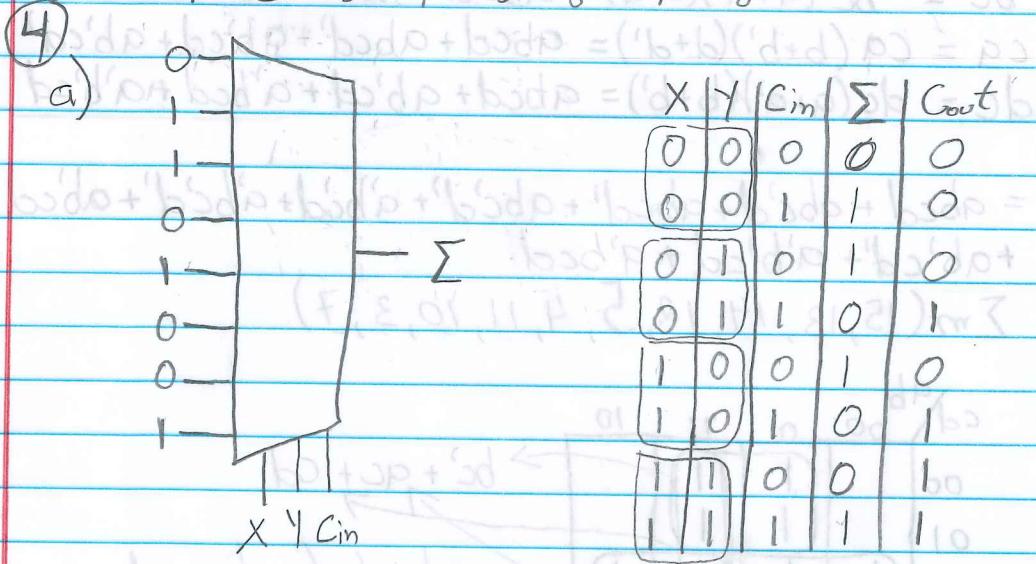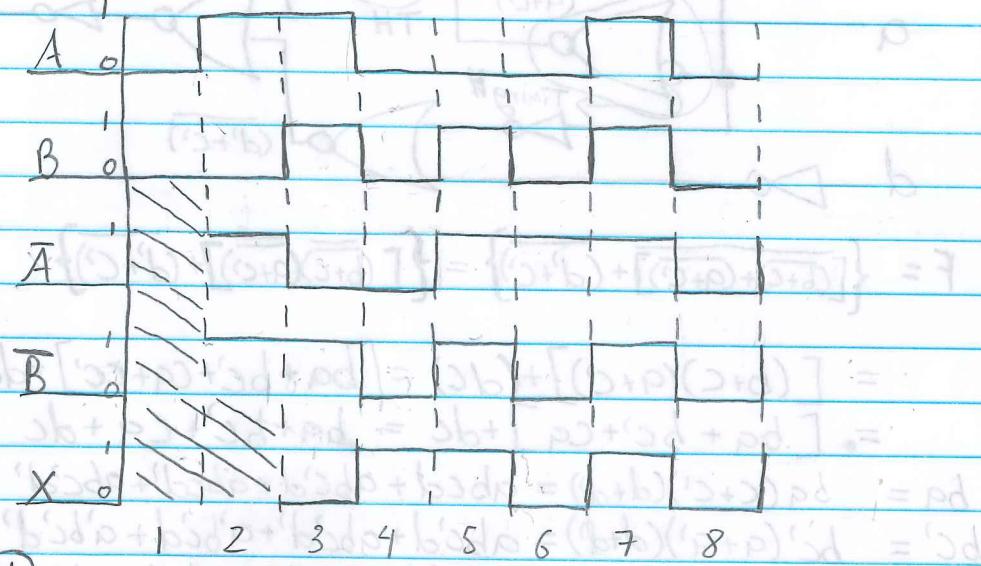


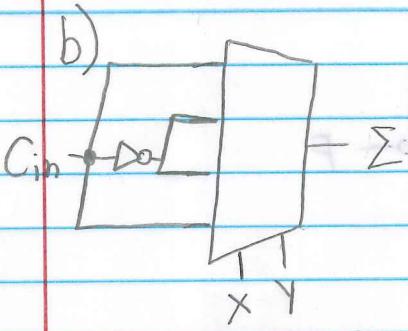


X	Y	Cin	Σ	Cout
0	0	0	0	0 } Cout = 0
0	0	1	1	0 } Cout = Cin
0	1	0	1	0 } Cout = 0
1	0	0	1	0 } Cout = Cin
1	0	1	0	1 } Cout = Cin
1	1	0	0	1 } Cout = 1
1	1	1	1	1 } Cout = 1

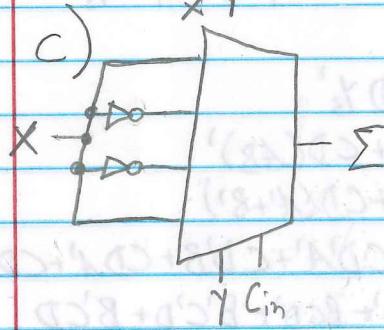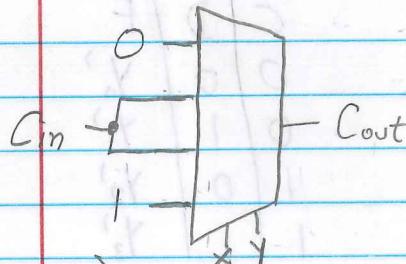

X	Y	Cin	Σ	Cout
0	0	0	0	0 } Cout = 0
0	0	1	0	0 } Cout = X
1	0	1	0	0 } Cout = X
1	1	0	1	1 } Cout = 1
0	0	1	0	0 } Cout = 0
0	1	0	1	0 } Cout = X
1	0	0	1	0 } Cout = X
1	1	1	1	1 } Cout = 1

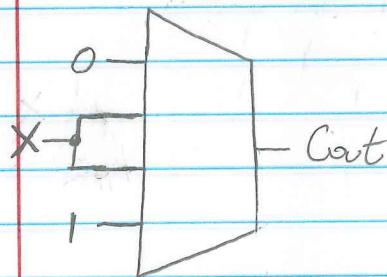

⑤

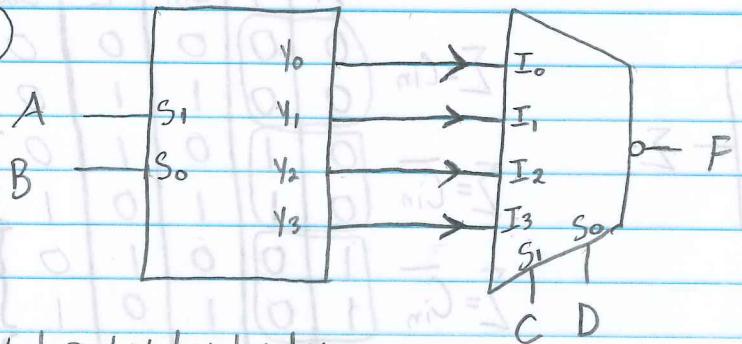

A	B	Y_0	Y_1	Y_2	Y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$\rightarrow Y_0 = A'B'$$

$$\rightarrow Y_1 = A'B$$

$$\rightarrow Y_2 = AB'$$

$$\rightarrow Y_3 = AB$$

C	D	F
0	0	Y_0'
0	1	Y_1'
1	0	Y_2'
1	1	Y_3'

$$F = C'D'Y_0' + C'DY_1' + CD'Y_2' + CDY_3'$$

$$F = C'D'(A'B')' + C'D(A'B)' + CD'(AB)' + CD(AB)'$$

$$F = C'D'(A+B) + C'D(A+B') + CD'(A+B) + CD(A+B')$$


$$F = C'D'A + C'D'B + C'DA + C'DB' + CD'A' + CD'B + CDA' + CDB'$$

$$F = AC'D' + AC'D + A'CD' + A'CD + BC'D' + BCD' + B'C'D + B'CD$$

$$F = AC'(D'+D) + A'C(D'+D) + BD'(C'+C) + B'D(C'+C)$$

$$F = AC + A'C + BD' + B'D$$

(6)

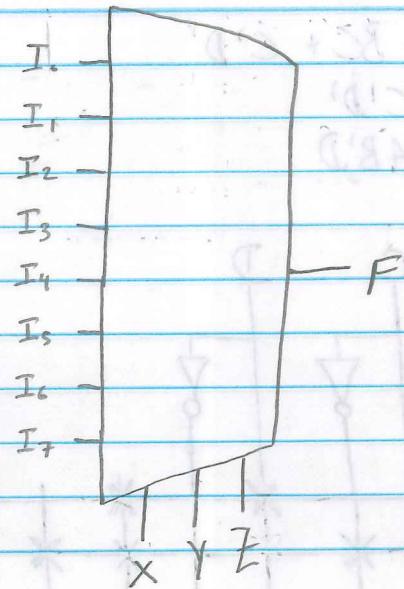

	X	Y	Z	F
I ₀	0	0	0	I ₀
I ₁	0	0	1	I ₁
I ₂	0	1	0	I ₂
I ₃	0	1	1	I ₃
I ₄	1	0	0	I ₄
I ₅	1	0	1	I ₅
I ₆	1	1	0	I ₆
I ₇	1	1	1	I ₇

$$F = I_0 \bar{X} \bar{Y} \bar{Z} + I_1 \bar{X} \bar{Y} Z + I_2 \bar{X} Y \bar{Z} + I_3 \bar{X} Y Z + I_4 X \bar{Y} \bar{Z} + I_5 X \bar{Y} Z \\ + I_6 X Y \bar{Z} + I_7 X Y Z$$

$$F = \bar{X} (\underbrace{I_0 \bar{Y} \bar{Z}}_1 + \underbrace{I_1 \bar{Y} Z}_2 + \underbrace{I_2 Y \bar{Z}}_3 + \underbrace{I_3 Y Z}_4) + X (\underbrace{I_4 \bar{Y} \bar{Z}}_5 + \underbrace{I_5 \bar{Y} Z}_6 + \underbrace{I_6 Y \bar{Z}}_7 + \underbrace{I_7 Y Z}_8)$$

AND Terms = 1 2 3 4 5 6 7 8


PAL Design on Logisim
Next Page

$$⑦ X = AB'D + A'C' + BC + C'D'$$

$$Y = A'C' + AC + C'D'$$

$$Z = CD + A'C' + AB'D$$

a)

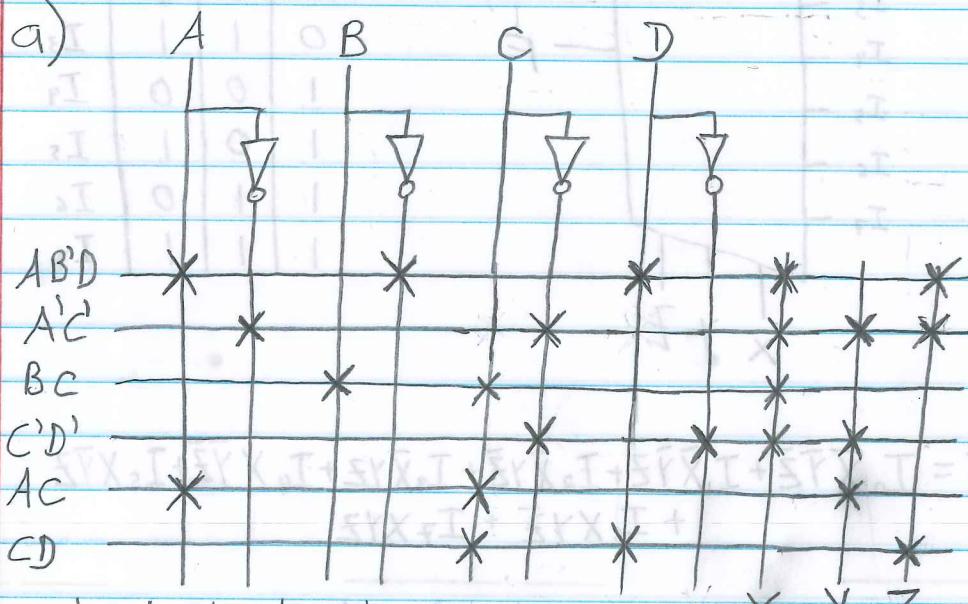

b)

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	1	1	1
0	1	0	1	1	1	1
0	1	1	0	1	0	0
0	1	1	1	1	0	1
1	0	0	0	1	1	0
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	1	1
1	1	0	0	1	1	0
1	1	0	1	0	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	1

FIVE STAR. ★★

FIVE STAR. ★★


FIVE STAR. ★★

FIVE STAR. ★★

Homework #4

Estheran Romeiro

U1680 3837

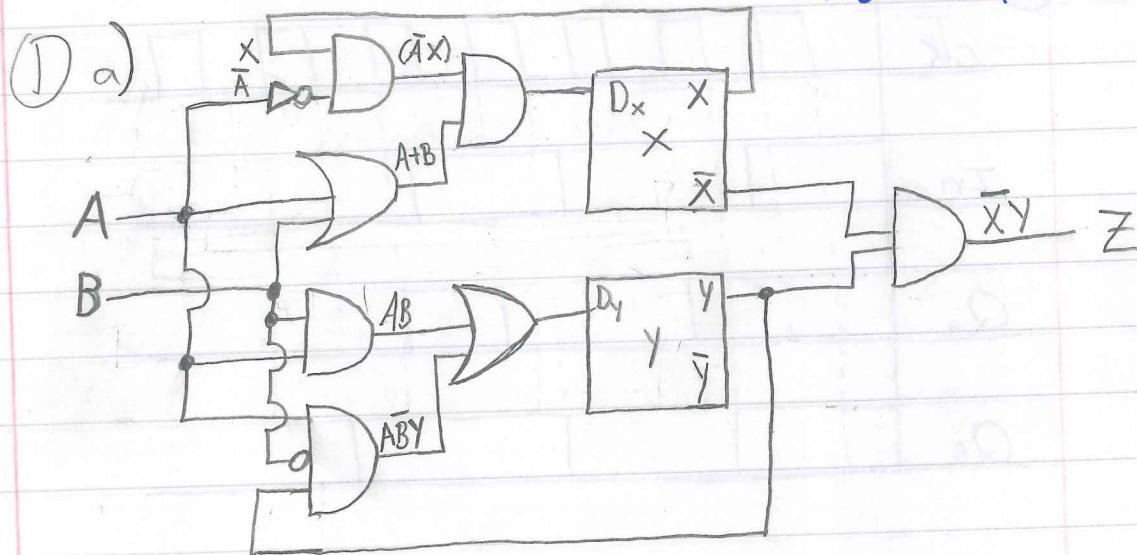

b)

	Current State	Inputs	Next State	OUT
S_0	X Y	A B	X^+ Y^+	Z
S_1	0 0	0 0	0 0	0 0
S_2	0 0	0 0	0 0	0 0
S_3	0 0	0 0	0 0	0 0


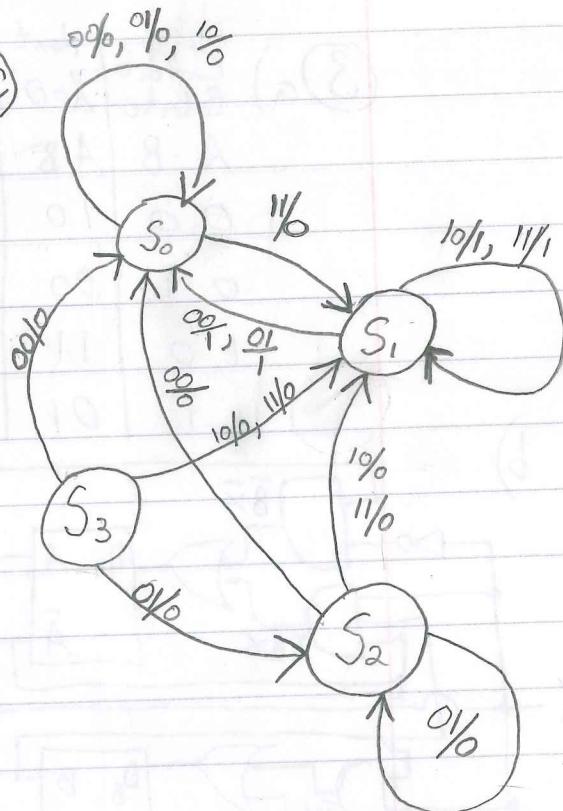


Diagram 2


PT# 2

②

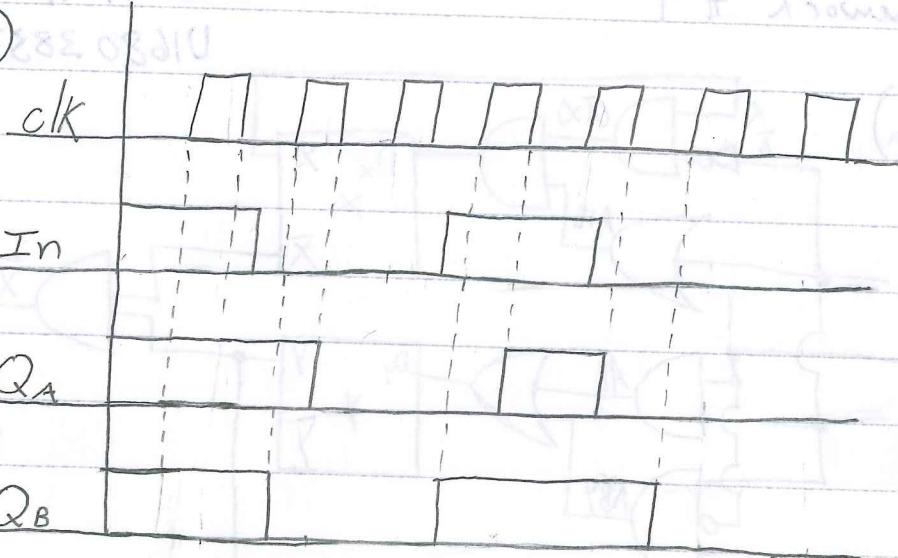

Current State	Next State		CS	Input	OUT	NS.
	X=0	X=1				
A B	AB	AB	X=0	X=1	AB	X ⁺ B ⁺
0 0	1 0	0 1	0	0	0 0	1 0
0 1	0 0	1 1	0	0	0 1	0 1
1 0	1 1	0 0	0	1	1 0	1 1
1 1	0 1	0 0	0	1	1 1	0 0

b)

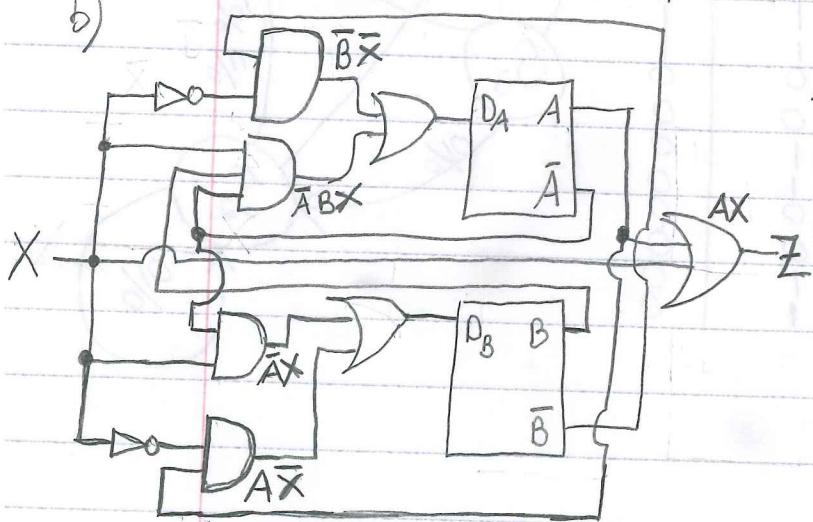

Z	A ⁺	B ⁺
AB	0 0	0 0
0 0	0 0	0 0
0 1	0 1	0 1
1 0	1 0	1 0
1 1	1 1	1 1

$Z = AX$ $A^+ = \bar{B}\bar{X} + \bar{A}B\bar{X}$ $B^+ = \bar{A}\bar{X} + \bar{A}\bar{X}$


Note: Could have used a XOR for D_B but chose not to.

(4)

IN	CS	NS	Q^+	
A B	Q	Q^+	Q	
0 0	0	1	0 00	0 1 11 10
0 0	1	0	0 00	0 0 11 00
0 1	0	0	1 0	0 0 0 0
1 0	0	0	0 0	
1 1	0	1	0	

$$Q^+ = \bar{A}\bar{B}\bar{Q} + \bar{A}B\bar{Q} + AB\bar{Q}$$

CS	NS	Input	
Q	Q^+	A B	
0	0	0 0 } XX	0 00 01 11 10
0	1	0 0 } XX	0 1 0 1 0 0
1	0	0 0 } XX	1 0 1 0 0 0
1	1	0 1 } 0 1	

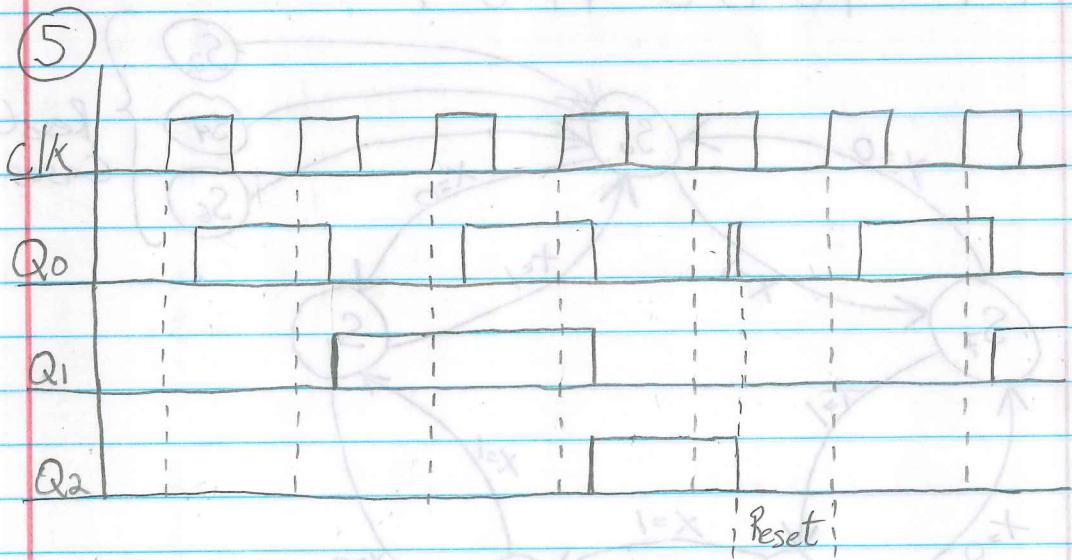


⑥ $X=0 : 0, 1, 3, 5, 7$

$X=1 : 7, 5, 3, 1, 0$

Return to 0 when in 2, 4, 6

CS	$NS \ X=0$	$NS \ X=1$
A	$A^+ B^+ C^+$	$A^+ B^+ C^+$
$S_0 \rightarrow 0 \ 0 \ 0$	0 0 1	1 1 1
$S_1 \rightarrow 0 \ 0 \ 1$	0 1 1	0 0 0
$S_2 \rightarrow 0 \ 1 \ 0$	0 0 0	0 0 0 → Reset Case
$S_3 \rightarrow 0 \ 1 \ 1$	1 0 1	0 0 1
$S_4 \rightarrow 1 \ 0 \ 0$	0 0 0	0 0 0 → Reset Case
$S_5 \rightarrow 1 \ 0 \ 1$	1 1 1	0 1 1
$S_6 \rightarrow 1 \ 1 \ 0$	0 0 0	0 0 0 → Reset Case
$S_7 \rightarrow 1 \ 1 \ 1$	0 0 0	1 0 1

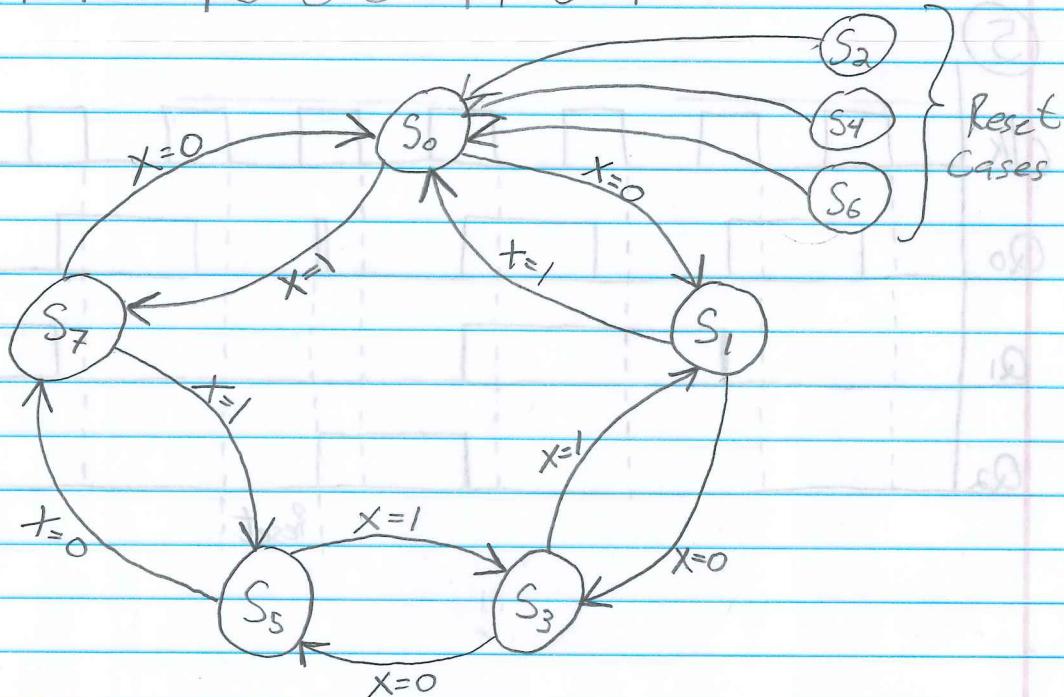


Esther van Romeiro
U16803837

Homework 5

① Inputs X_1, X_2 & output Z

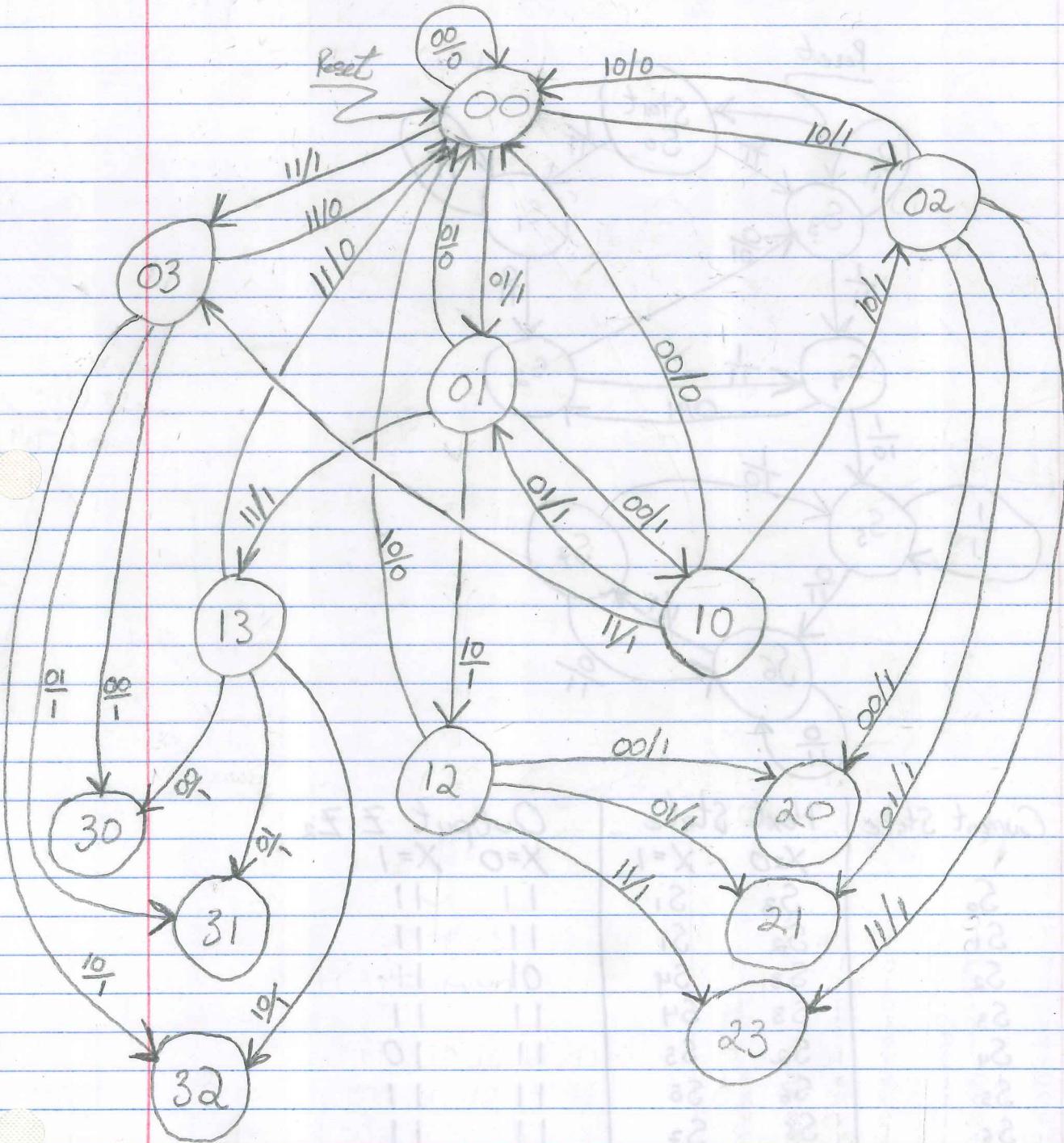Outputs $Z=1$ in all cases except on consecutive




oriental circuit 23
F288 0821 U

2) Knowsolt H

② Example Input: 10011001101011

Z1 out: 11011111111111


Z2 out: 1111011011110

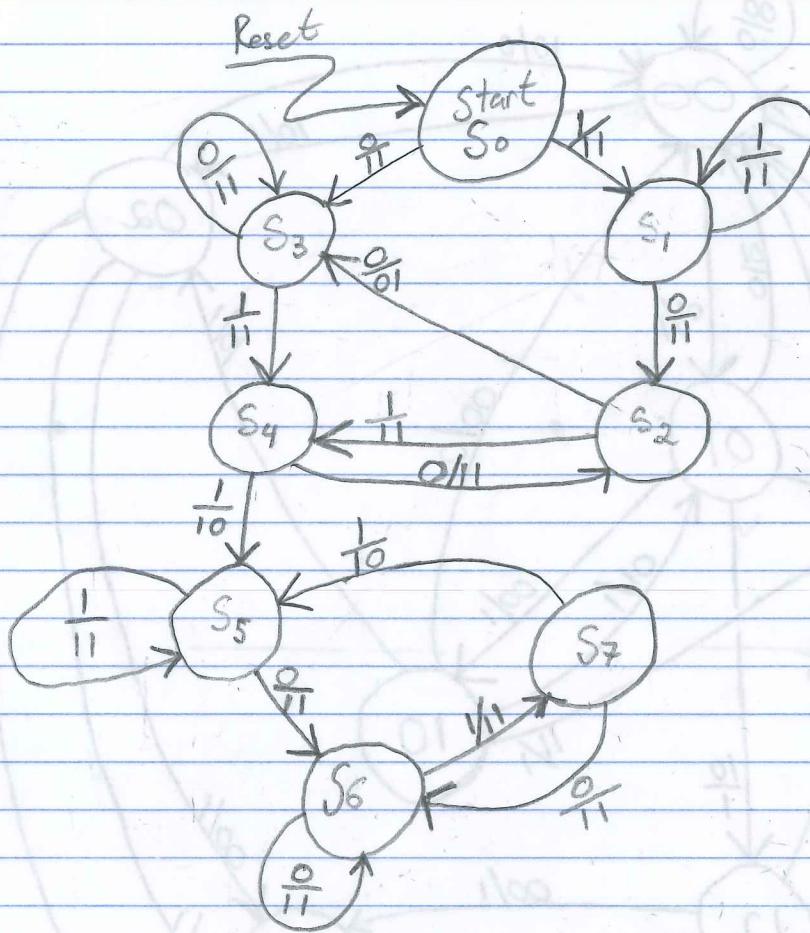

Current State	Next State		Output Z ₁ , Z ₂	
	X=0	X=1	X=0	X=1
S ₀	S ₃	S ₁	11	11
S ₁	S ₂	S ₁	11	11
S ₂	S ₃	S ₄	01	11
S ₃	S ₃	S ₄	11	11
S ₄	S ₂	S ₅	11	10
S ₅	S ₆	S ₅	11	11
S ₆	S ₆	S ₇	11	11
S ₇	S ₆	S ₅	11	10

③ Moore Machine inputs X, outputs Y & Z

Ex: X: 0011010011011
YZ: 00120111201012

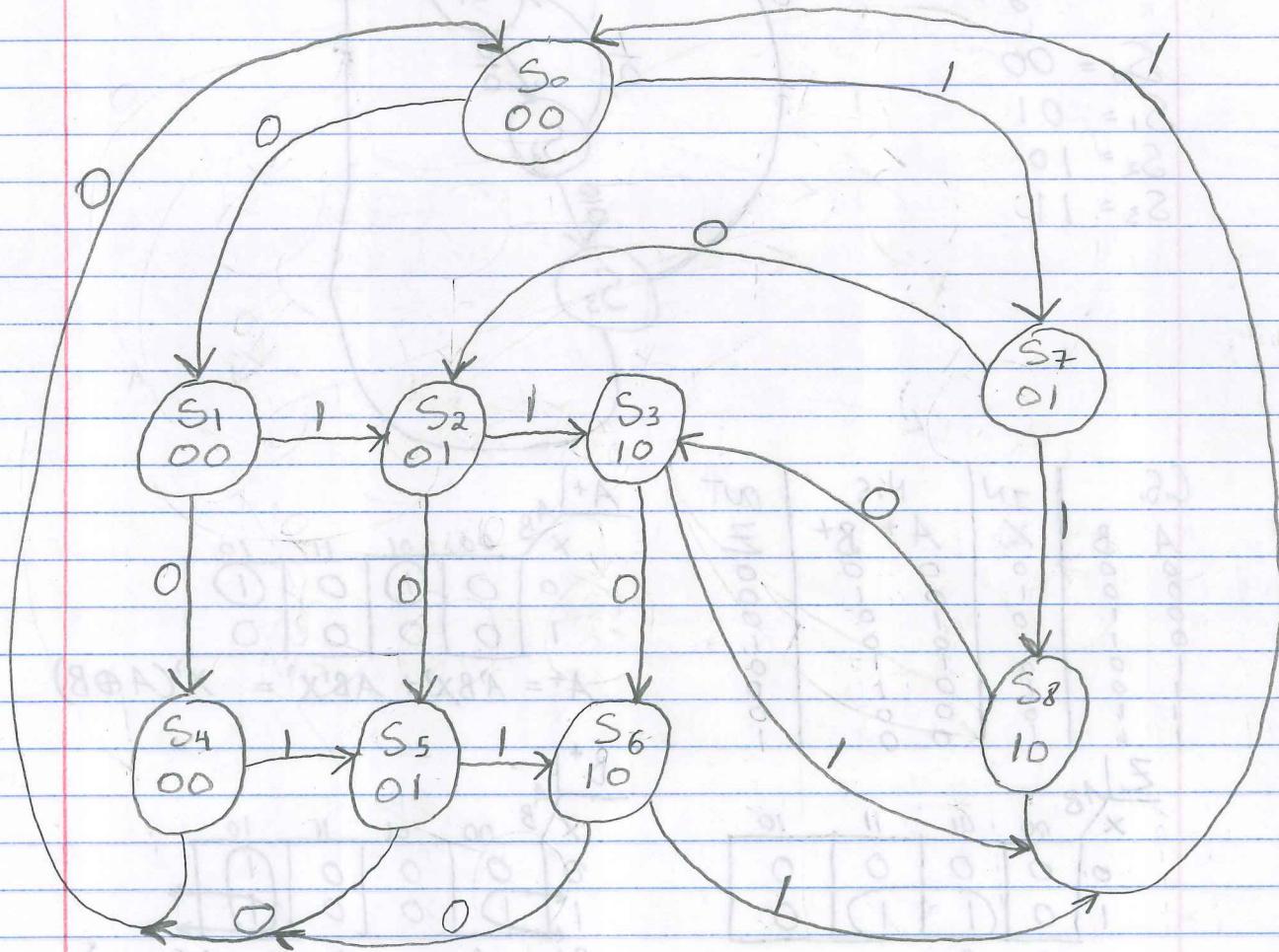

Current State	X=0	X=1	Output YZ
S ₀	S ₁	S ₇	00
S ₁	S ₄	S ₂	00
S ₂	S ₅	S ₃	01
S ₃	S ₇	S ₀	10
S ₄	S ₀	S ₅	00
S ₅	S ₀	S ₆	01
S ₆	S ₀	S ₀	10
S ₇	S ₂	S ₈	01
S ₈	S ₃	S ₀	10

$X = 010110010010110$
 $out = 000010000010010$

1010P1

(4)


State Assignment

$$S_0 = 00$$

$$S_1 = 01$$

$$S_2 = 10$$

$$S_3 = 11$$

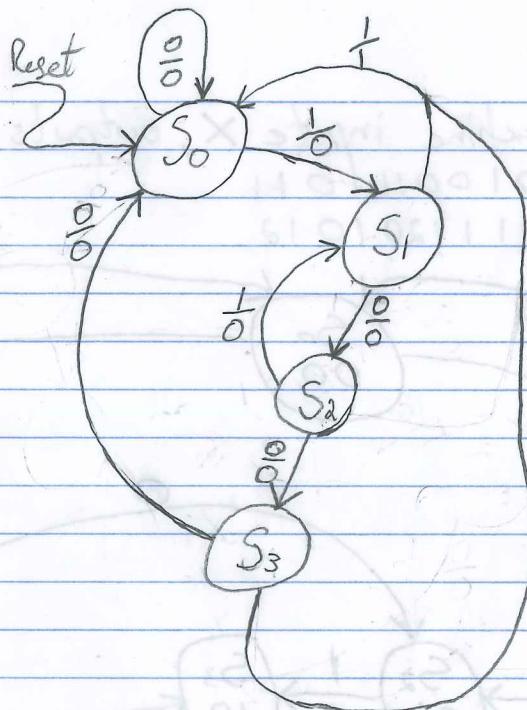

C.S.	IN	N.S	OUT
A 0	B 0	X 0	$A + B^+$ 0
0	0	0	0
0	1	0	1
0	1	0	0
1	0	0	1
1	0	0	0
1	1	0	0
1	1	0	1

A	B	Z
x	00	00
0	01	01
0	11	11
0	10	10
1	00	00
1	01	01
1	11	11
1	10	10


$A^+ = \bar{A}'Bx^+ + AB^+X = X'(A \oplus B)$

Z	A	B	00	01	11	10
x	0	0	0	0	0	0
0	0	0	0	0	0	0
1	0	1	1	1	0	0

$$Z = BX$$


B	A	Z
x	00	00
0	01	01
0	11	11
0	10	10
1	00	00
1	01	01
1	00	00
1	01	01

$$B^+ = B^+X + AB^+ = B^+(X+A)$$

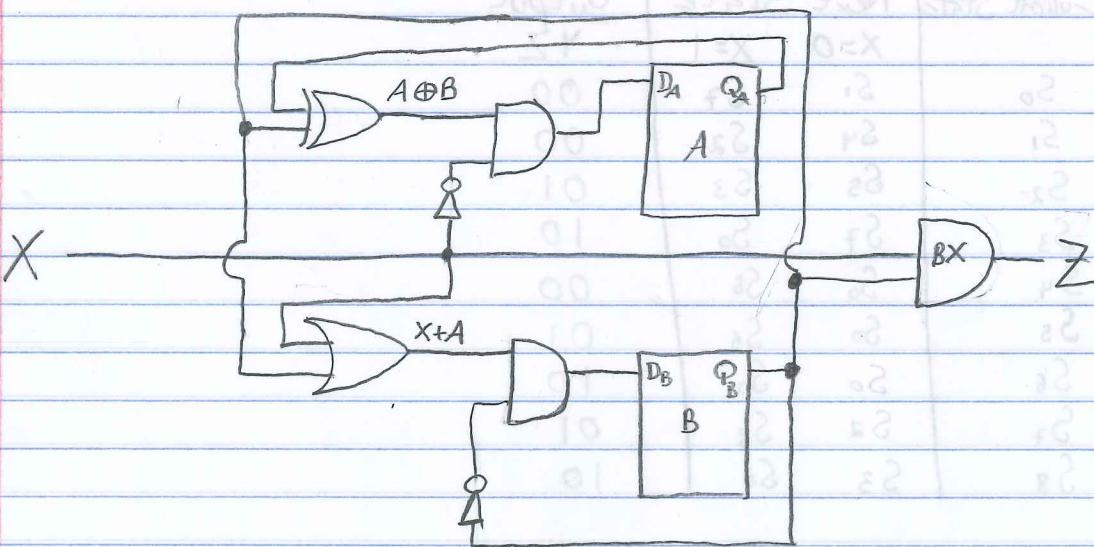

C.S.	N.S.		OUT	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₄	X	X
S ₁	S ₂	S ₈	X	X
S ₂	S ₃	S ₉	X	X
S ₃	S ₀	S ₀	1	0
S ₄	S ₅	S ₇	X	X
S ₅	S ₆	S ₁₀	X	X
S ₆	S ₀	S ₀	0	1
S ₇	S ₁₀	S ₉	X	X
S ₈	S ₉	S ₁₀	X	X
S ₉	S ₀	—	0	X
S ₁₀	S ₀	—	1	X

O- 0000	(5)	A	B	C	D	OUT Z
1- 0001		0	0	0	0	1
2- 0010		0	0	1	0	0
3- 0011		0	1	0	1	1
4- 0100		0	1	1	0	0
5- 0101		1	0	0	0	1
6- 0110		1	0	1	0	X
7- 0111		1	1	0	0	X
8- 1000		1	1	0	1	X
9- 1001		1	1	1	0	X

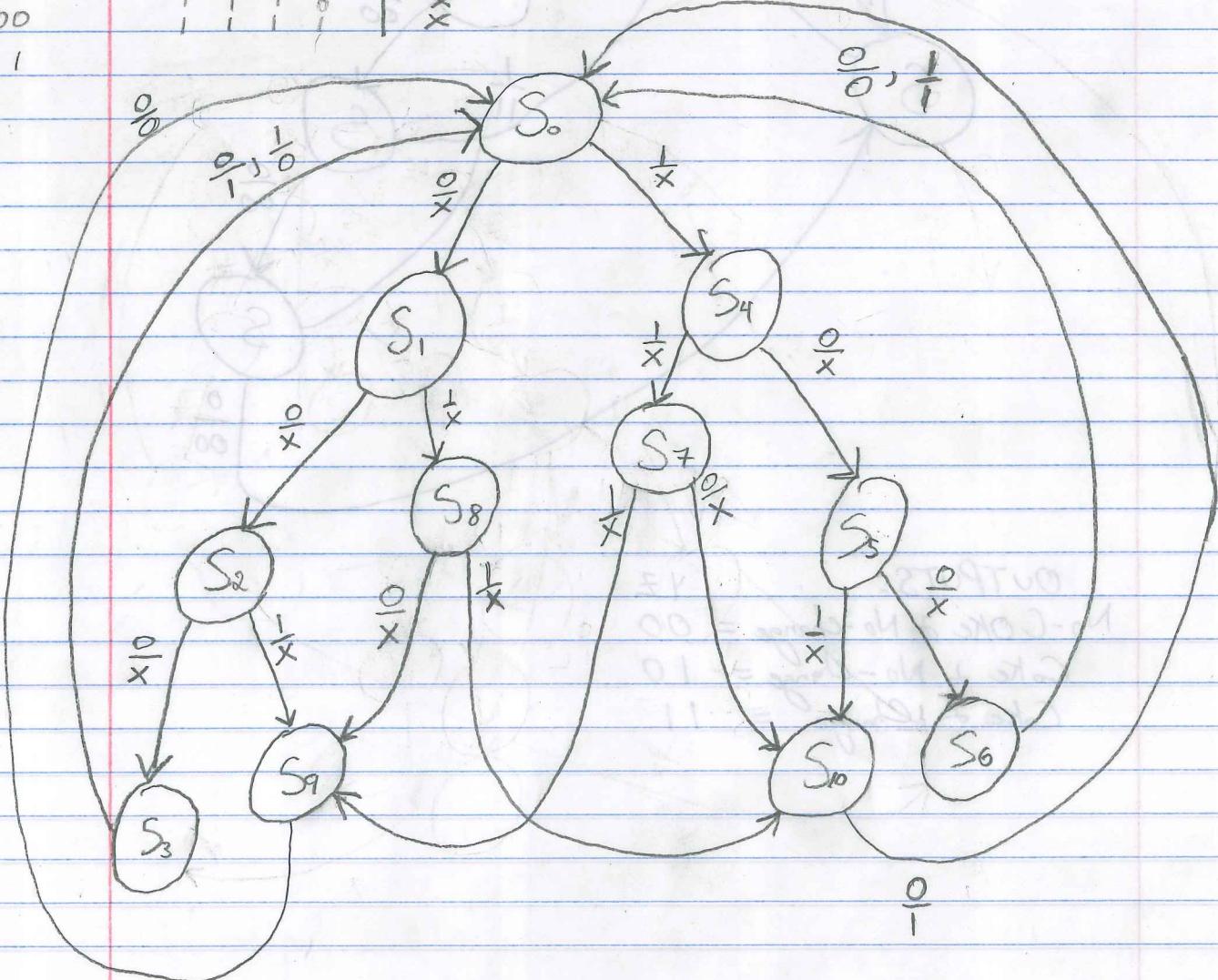

TUO	2H	1	2.0
=x	0=x	1=x	0=x
X	X	X	X
X	X	X	X
X	X	X	X


⑥

inputs: Dollar = 1, Quarter = 0

outputs: Coke = 1, No Coke = 0, Change = 0, No Change = 0

* Output Y=Coke

* Output Z=Change

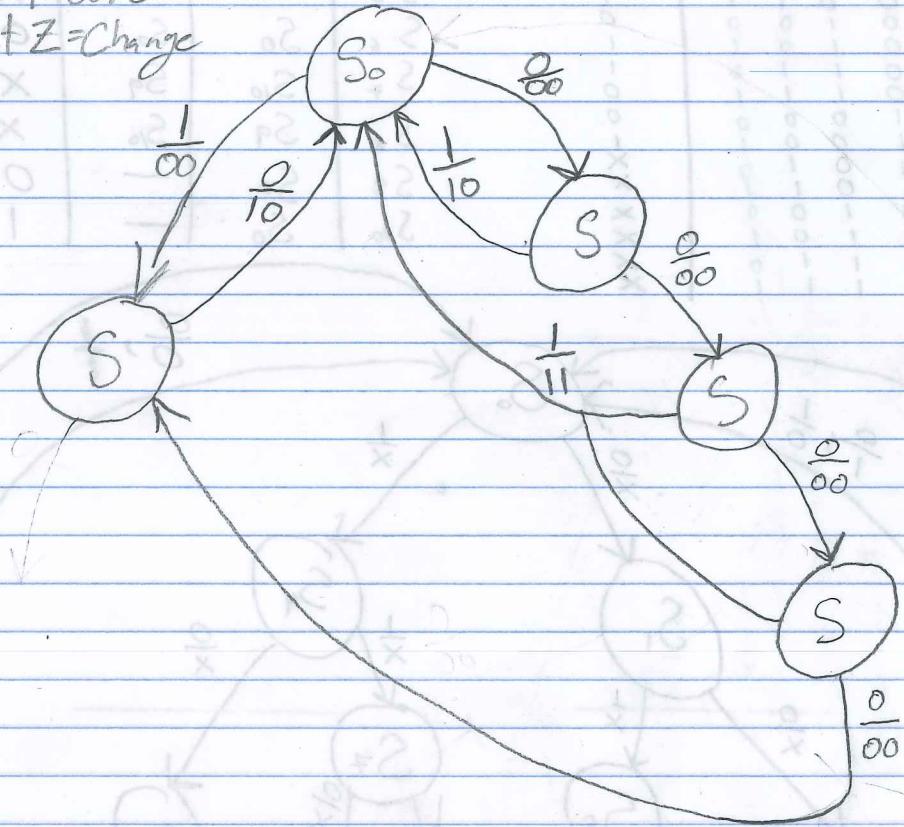

Format
 $\frac{X_{in}}{YZ}$

OUTPUTS: YZ

No-Coke & No-change = 00


Coke & No-change = 10

Coke & Change = 11

Homework #6

Estheran Romeiro
U16803837


1

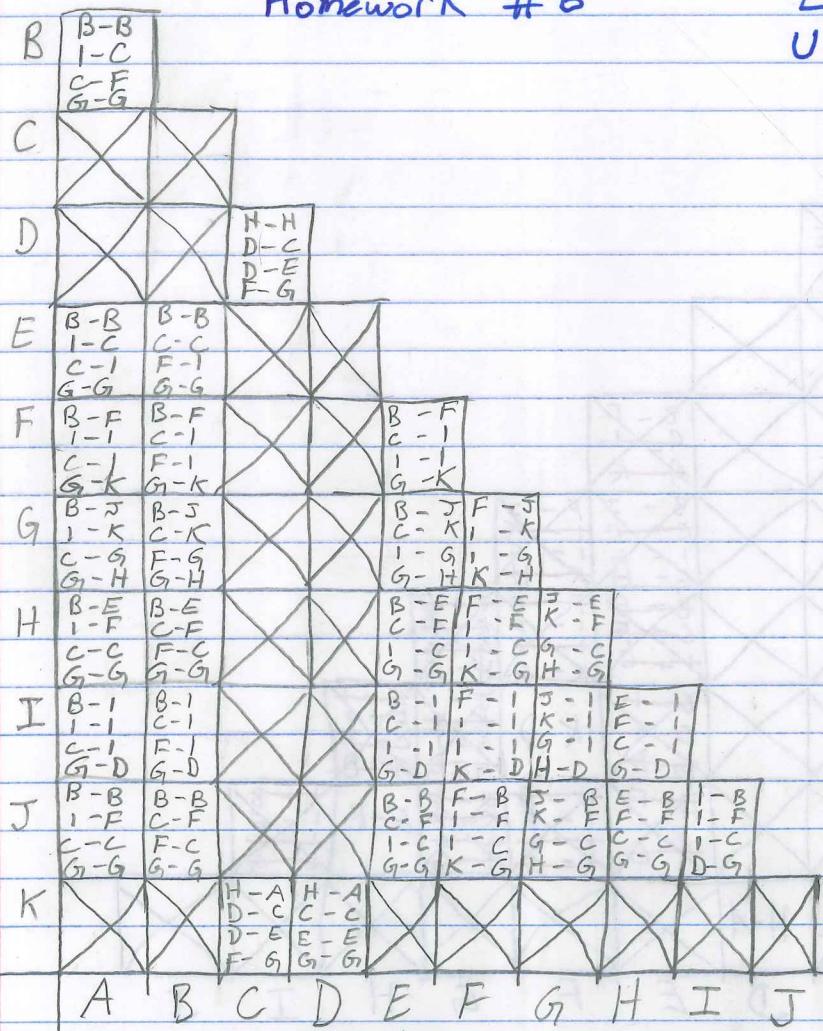

Eliminate all repetitions → Cleaned up
i.e. B-B X = 1 Chart

i.e. B-B

Chart

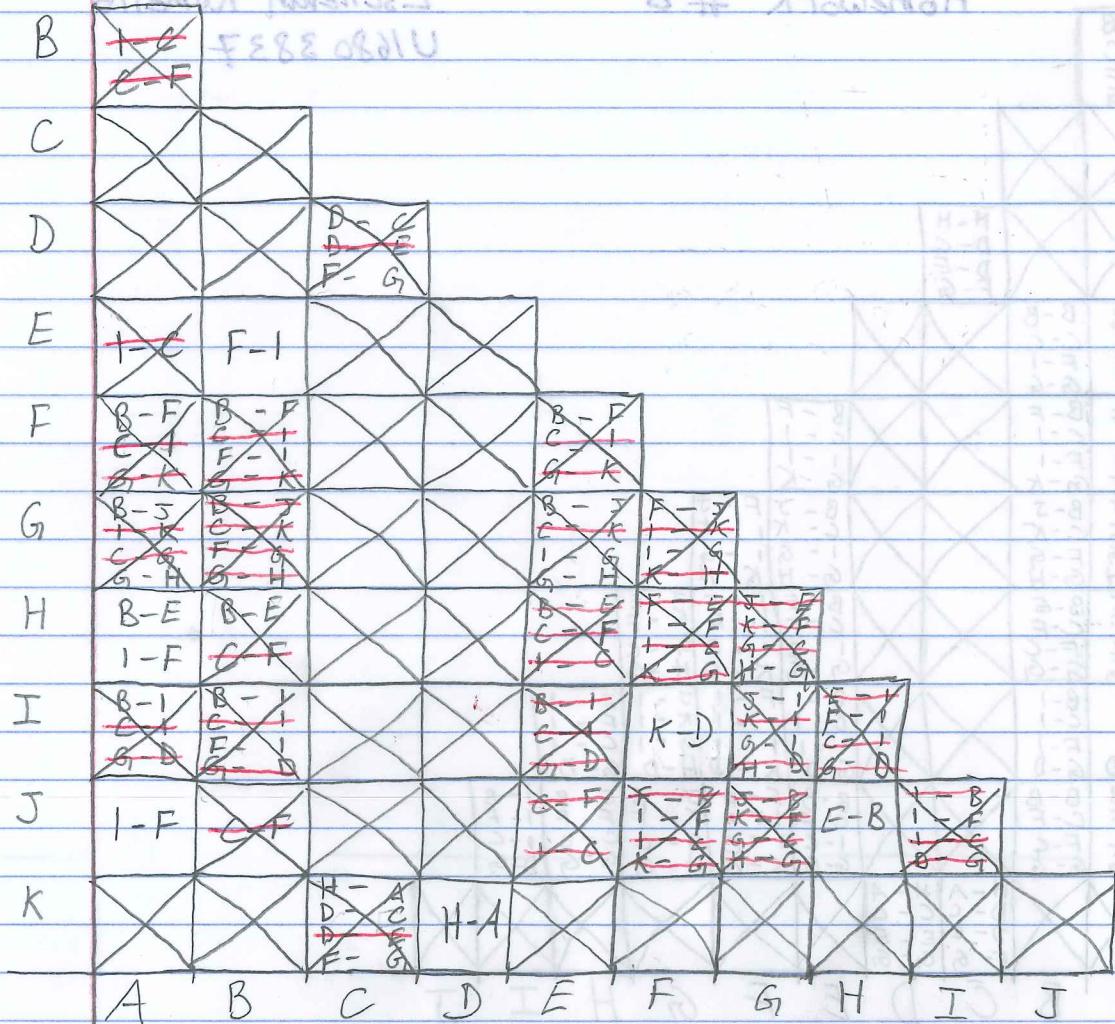

$A \equiv H$ if $B \equiv E$ ✓ and $I \equiv F$ ✓

$A \equiv J$ if $I \equiv F$ ✓

$B \equiv E$ if $I \equiv F$ ✓

$D \equiv K$ if $H \equiv A$ ✓

$I \equiv F$ if $K \equiv D$ ✓

$\therefore A \equiv H \equiv J$

$B \equiv E$

$D \equiv K$

$I \equiv F$

Reduced State Table

Present State	NEXT STATE				Output
	XY=00	XY=01	XY=11	XY=10	
A	B	I	C	G	0
B	B	C	I	G	0
C	A	D	D	I	1
D	A	C	B	G	1
G	A	D	G	A	0
I	I	I	I	D	0

(2)

B	B-G				
C	F-C	F-C			
	B-G				
D	F-A	F-A	C-A		
		G-B	G-B		
E					
F	B-A	F-A	C-A	B-A	
		G-A	G-A		
G	B-A	G-A	C-F	A-F	A-F
			G-A	B-A	
	A	B	C	D	E
					F

$A \equiv B$ if $B \equiv G \checkmark$

$A \equiv C$ if $F \equiv C \checkmark$ and $B \equiv G \checkmark$

$A \equiv D$ if $F \equiv A \checkmark$

$A \equiv F$ if $B \equiv A \checkmark$

$A \equiv G$ if $B \equiv A \checkmark$

$B \equiv C$ if $F \equiv C \checkmark$

$B \equiv D$ if $F \equiv A \checkmark$ and $G \equiv B \checkmark$

$B \equiv F$ if $F \equiv A \checkmark$ and $G \equiv A \checkmark$

$B \equiv G$ if $G \equiv A \checkmark$

$C \equiv D$ if $C \equiv A \checkmark$ and $G \equiv B \checkmark$

$C \equiv F$ if $C \equiv A \checkmark$ and $G \equiv A \checkmark$

$C \equiv G$ if $C \equiv F \checkmark$ and $G \equiv A \checkmark$

$D \equiv F$ if $B \equiv A \checkmark$

$D \equiv G$ if $A \equiv F \checkmark$ and $B \equiv A \checkmark$

$F \equiv G$ if $A \equiv F \checkmark$

$A \equiv B \equiv C \equiv D \equiv F \equiv G$

$B \equiv C \equiv D \equiv F \equiv G$

$C \equiv D \equiv F \equiv G$

$D \equiv F \equiv G$

$F \equiv G$

$\therefore A \equiv B \equiv C \equiv D \equiv F \equiv G$

E

Reduced State Table

Present State	Next State	Output
A	X=0 X=1	X=0 X=1
E	A A	0 0

③ Guideline 1: States which have the same next states for a given input \rightarrow columns for each input
 $(A, C) \times 2 \quad (B, C) \times 2 \quad (A, D)$

Guideline 2: States which are the next states of a given state \rightarrow row for each input
 $(A, C) \quad (B, D) \quad (A, B, D) \quad (D, A, C)$

Guidelines 3: States with the same outputs for a given input \rightarrow row of outputs match
 (A, D)

Preference is given to guideline 1 conditions over guideline 2. Furthermore, conditions that are required 2 or more times are given preference over those that are only required once

Q_2	Q_1
0	1
A	C
D	B

$$A = 00, D = 01, C = 10, B = 11$$

Original } \rightarrow Table

$X_1 X_2$	00	01	11	10
00	A	D	B	A
01	A	D	D	A
11	C	A	B	B
10	C	C	D	D

$X_1 X_2$	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	1	0	1	1
10	1	1	0	0

$X_1 X_2$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	0	1	1
10	0	0	1	1

$$Q_i^+ = Q_1 \bar{Q}_2 X_i + \bar{Q}_1 X_i \bar{X}_2 + Q_1 X_i X_2 + Q_1 Q_2 \bar{X}_1 \bar{X}_2$$

$$Q_2^+ = Q_2 \bar{X}_1 + Q_1 X_1$$

\Rightarrow KMAPS

Z_0	$Q_1 Q_2$	A	B	C
$X_1 X_2$	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	0
10	0	0	1	0

Z_1	$Q_1 Q_2$	A	D	B	C
$X_1 X_2$	00	01	11	10	
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	0
10	1	1	1	1	0

$$Z_0 = Q_1 Q_2 + Q_1 \bar{X}_1$$

$$Z_1 = \bar{Q}_1 + \bar{X}_1 + Q_1 Q_2$$

(4) $Q_A^+ = X(A+B+C+D)$ where FF $Q_A = A$
 $Q_B^+ = \bar{X}A$ " $Q_B = B$
 $Q_C^+ = \bar{X}B$ " $Q_C = C$
 $Q_D^+ = \bar{X}(C+D)$ " $Q_D = D$



$$\therefore Q_A^+ = X(Q_A + Q_B + Q_C + Q_D)$$


$$Q_B^+ = \bar{X}Q_A$$

$$Q_C^+ = \bar{X}Q_B$$

$$Q_D^+ = \bar{X}(Q_C + Q_B)$$


$$Z = XQ_C$$

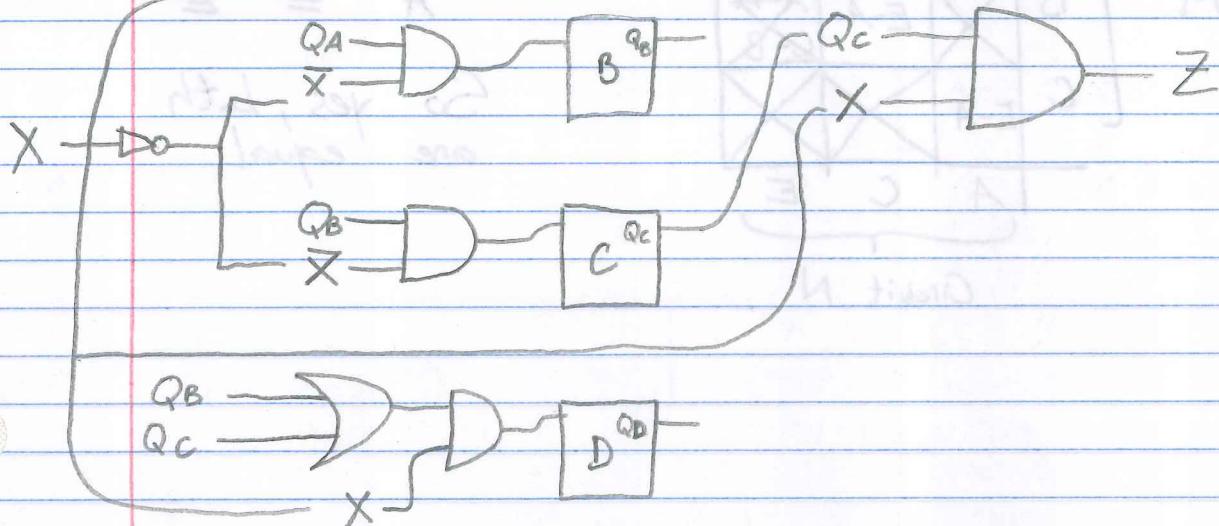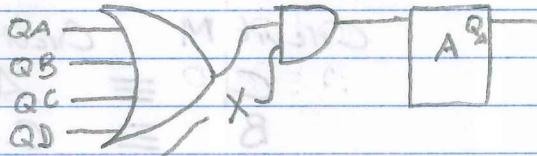

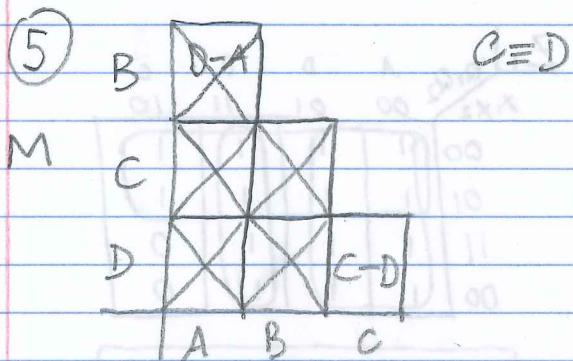


Reduced State Table M

Present State	Next State	Out
	$X=0$	$X=1$
M	C	Z
C	B	0
B	A	0
D	A	1

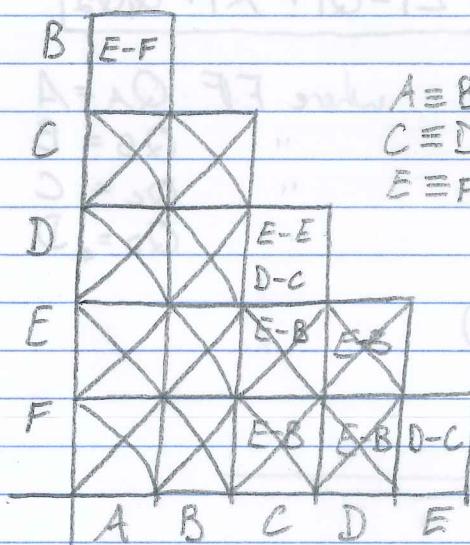

Reduced State Table N

Present State	Next State	Out
	$X=0$	$X=1$
A	E	Z
C	E	1
E	C	0
F	A	0

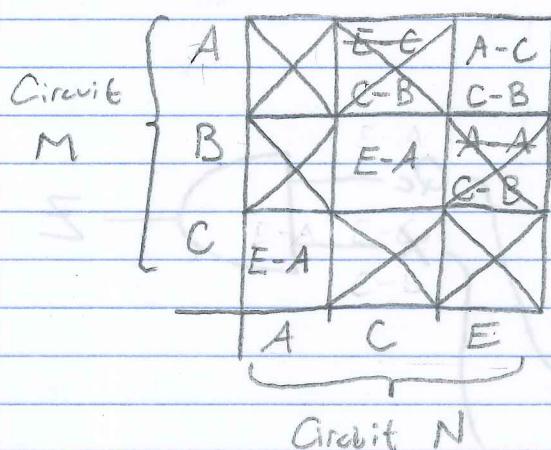

Circuit M Circuit N

$$\begin{array}{ll} C & \equiv A \\ B & \equiv C \\ A & \equiv E \end{array}$$

So yes, both
are equal